

RTTY

March 1979

JOURNAL

VOLUME 27 NO 3

75 CENTS



CONTENTS

TH-5 TELETYPE TERMINAL UNIT REVISITED

HAM HELPS

1978 SARTG CONTEST RESULTS

SECOND LOOK - YAESU FR101 CONVERSION

Subscription Rates

RTTY JOURNAL

Dee Crumpton, Editor & Publisher
P.O. Box RY
Cardiff by the Sea, CA. 92007

The RTTY JOURNAL
SUBSCRIPTION RATES

RATES AS OF OCTOBER 1, 1978 WILL BE:

US - \$5.00 per year.
CANADA and MEXICO - \$6.50 per year
Air Mail \$7.50 per year.

FOREIGN AIR MAIL \$12.00 per year.

Published 10 times per year, May-June
July-August are combined issues.
Second Class permit Encinitas
California 92024.

Subscription rates above.

Business Offices
1155 Arden Drive
Encinitas, California 92024

POSTMASTER SEND FORM 3579 to
Post Office Box 179
Cardiff by the Sea, California 92007

New subscriptions and classified ads
are cash in advance as we have no
method for billing. New subscriptions
will be started with the current issue

Please do not ask us to start any
further back than this. The JOURNAL
is mailed about the 20th of the month
preceding the dated month. May and
June are combined in one issue and
July and August are combined in one
issue.

BACK ISSUES

A duplicate of any back issue may be ob-
tained from R. Wilson, 4011 Clearview Dr.,
Cedar Falls, IA. 50613. \$1.00 pp. Reprints of
all UART articles, \$2.00 pp.

RTTY JOURNAL

PO Box RY

Cardiff by the Sea, CA. 92007

**FOREIGN SUBSCRIPTION
MANAGERS**

EUROPE

Jean F. Hurtaud - FBXT
Chillac
16480 Brossac, FRANCE

AUSTRALIA

Norman Wilson - VK4NP
P.O. Box - 81 a
Albion Brisbane
Queensland 4010-AUSTRALIA

THE RTTY JOURNAL AIR SHIPS TO THE FOLLOWING
FOREIGN SUBSCRIPTION MANAGERS. CONTACT THEM
FOR RATES IN THEIR TERRITORIES.

ENGLAND

Arthur Owen - G2FUD
Gwenarth
184 Hale Road
Hale, Cheshire ENGLAND

Japan


Toshio Hotta - JA2EFV
4-5-11 Tomida
Yokkaichi City
Mie-Pref., JAPAN 512

BUY YOUR RTTY BEGINNERS HANDBOOK \$4.50

• RTTY-DX •

SKIP PRINSEN WB6CYA 714-276-3182

3611 Merrimac, San Diego, Calif. 92117

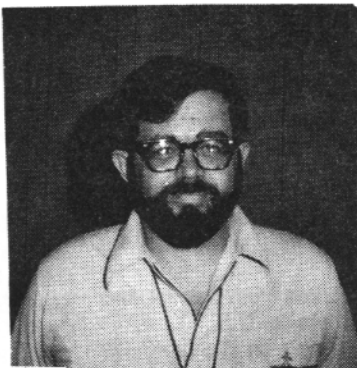

Greetings to all...

I recently received the December 78 copy of "AREWISE" the official Publication of the Australian National Amateur Radio Teleprinter Society. This rapidly growing publication is excellent with articles on micros, VARTS and news in general about members and RTTY. I found no information on joining their organization but have their address:

The Secretary
c/o W.I.C. 14 Atchison Street
Crows Nest, N.S.W. 2065
Australia

From "AREWISE" was one note of interest to the DX'er.

ZE1CE is a very interesting station, it is a repeater in Rhodesia, but you can work through it if you know how. The frequency is 14075KHZ, and you have to challenge it to work through it such as...ZE1CE - S DE VK2SG 1614Z 78/11/12 R CQ DE VK2SG - SYDNEY in SYDNEY K DE VK2SG NNNN.

If there is any one around they will then answer you through the repeater. It is a bit slow working that way, and if you can hear the station direct you may then work on the frequency but you do not give the time and date, nor do you finish up with NNNN. The repeater will remain quiet until you challenge it again. It will receive any message for you and store it for 24 hours. After the 24 hours it erases the message but retains your callsign and the callsign of the station that you called and informs you that there has been a message. This is working DX a different way, slow, but different. You must try it sometime "AREWISE."

Klaus K. Zielski, DF7FB, P.O. Box 1147 D-6455 Erlensee 1, F.R.G. has taken over the chores of the traffic manager of the DARC for RTTY - purposes. Klaus is looking for information that he can use in his local bulletins and publications. Send anything that you can to assist Klaus in his new endeavor to the address above.

Bruce Frahm K0BJ now settled aboard the ship "Yankee Trader" (we hope) writes, "the ship "Yankee trader" will be leaving the Bahamas on 15 February for her 9th world cruise. Three hams will be

aboard, K5UC, N1DX (ex HS2B1G/KA6DX) and myself, K0BJ ex WA0TAS. I haven't met the other hams in person yet and this note is not speaking for their plans, only mine. I will have TS820, remote VFO, Kleinschmidt TTY and ST5000 TU for RTTY, and will be using dipoles, and possibly a beam antenna for IMM and DX operations during Feb. 15-Dec. 15 1979. I may also guest operate at some stops.

Enclosed is the 1977 itinerary, which will be similar to our route and dates for this years cruise, but not identical. I have marked operations that I intend to make with a dash in front of the name of the port, and many of the others will be possibly showing up. The main emphasis at many of the semi rare spots will be RTTY, and the other times will be given to CW, SSB, low band or whatever is felt is the greatest need from that area. It must be emphasized that this is a sightseeing trip, not a DX pedition and most stops are brief in nature, but when possible I will be trying to work a maximum number of feist ZS0'S. RTTY action will be at 090xmit, tuning up or down on transceive; CW will be around 025 QSX up/down or transceive and fone at low end of the bavelts that for DX Spots. Shipboard operations will be largely 14313, 14265 14030 and 21360.

QSL's go to W0PAH with SASE/SAE IRC no contributions are solicited. I hold licenses for K0BJ/VP2V, K0BJ/C6A and VR6BJ. 5Z4 and CE0 are hopefully on the way, and many others will be applied for in person. Hope to work many of the guys this year from some interesting spots 73.

See Page # 13 Bruce

John Wood WB2VTD claims first RTTY QSO with South Pole on 13 Jan 79 with KC4AAA. I am not sure but believe that other south pole stations have been worked. I worked KC4AAD but still have not received a QSL card from a year ago. Any takes that can top that one?

Here is another one that is a first, W1MX the M.I.T. Radio Society (Massachusetts Institute of technology) has now worked all continents on all FIVE bands that is a

real tough one. Congrats to the operators at W1MX who have been K1MK (WA1RJK), W1XG (W2QHQ) WA2EYC, WB2CWQ, WB2MZE, WA4TTG, K85H, N0AL, and W0UC (WA0UCU) great work guys.

Contest logs were accepted for CARTG until 31 January 1979 due to the postal strike delaying the mails. May logs were returned to sender so it will be awhile yet until we get the results of the CARTG.

From Hal W9RY comes good news for those who might need a QSL card for QSO's with ON0NI. Sigge became a silent key in May of 1977. OH2LA now has Sigge's log books and QSL cards and will QSL to all. Don't forget the IRC's fellas and a note of thanks goes to Toivo Sorvali, Silmakiya 3, SF-00720 Helsinki 72, Finland.

The S.A.R.L. has set up a fund for handicapped hams in the names of Sigurd and Bjorn Mansnerus. Anyone wishing to donate to their foundation may do so by sending donations to SARL P.O. Box 306 00101 Helsinki 10 Finland.

Franco Fanti I4LCF, Via Dallolio n19, Bologna, Italy, writes:

"I do not remember if I have informed you of the good prizes offered by the I.A.T.G. for the Campionato Mondiale RTTY 1978 (score of BARTG - CARTG - SARTG - WAEDC - Giant RTTY Contest)."

"The first prize is the computer offered by the General Processor, a firm of computers of Florence, Computer called Child Z value Lire 700,000."

This prize is for the RTTY'er that has proved to have used home made equipment in the computer field in the contest RTTY or have introduced original modification in commercial equipment."

"This Campionato Mondiale RTTY 1978 is finished with the Giant Flash Contest (I am receiving in this moment the final score) and I ask your publicity on RTTY Journal for receive documentation for the computer prize."

"For the Campionato RTTY not is necessary submit documentation but for the computer prize is necessary this. Take note that not is important for this prize the position in the final score, but is necessary the prove of the use of this new

CONT. FROM PAGE 3

techniques."

Many thanks in advance for your help. Best 73s" Signed Franco Fanti I4LCF.

Here is a listing of some of the active stations that have been worked or noted on the barrels during the past few weeks.

K4GMH/VQ9 on Diego Garcia QSL via his stateside QTH.

9V1SI has been worked from Europe and only heard very weak in the U.S.

YB0YE has been seen on the band (20 meters) but not very strong.

VE6GBU/SU has not been able to get on RTTY due to equipment problems. He has parts on the way from Germany so watch for Willie.

ON7AZ the only non-club station on from Artwerp his name is ETIENNE.

ON6IA a new one from Belgium name ANTON.

4Z4KB Ran has good signals from Israel. SV1AB George QSL via box 564 in Athens.

OH0JN Ove. A new one and the only RTTY station from alnd Island.

5ZART Hermann in Germany only.

AL7J Ron from Anchorage with 599 sigs into Europe.

OD5JW Wassim in Lebanon.

GV5TU John very active with strong sigs on 10 mtrs.

Other stations printed were PY2YFG, DJ7YR, PA3AEI, DM2EDL, HB7NG, F5DE, XE2DH, ZP5CD, DK1BX, DZ2X, CP6EE, YV5ZZ, and CE3CF.

Inputs this month came from IS0ESS, WA3IKK, W3KV, K7BV, and W9RY.

73 de Skip.

HAM HELPS

Phillip Shaffer, 6815 N.E. 204th St., Bothell, Wa. 98011 needs information about how to build RTTY demodulators and getting started in RTTY in general. He also needs to know where to find parts for Model 19 and 15 machines and 11/16th in paper tape. Also paper for both friction and sprocket feed machines. He needs paper tape reader brushes desperately. Any one that can help him?

A.M. Fitzgerald, 14 Caruer Street, Springfield, Mass. 01108, Phone 413-734-4109 is interested in building a complete RTTY Station with a video monitor. He doesn't have a strong electronic background but wants to give it a stab. He also wants to include a morse code sender and receive it to show on a video monitor.

Donald Collins WA8, WQT, 412 Wooster Rd., Millersburg, Ohio 44654, would like to know how to transmit FSK with a swan 500CX using a HALST5.

Kontest Korner

BARTG 24th-26th March rules in Feb. 79 Journal

DAFG 5 May 1979 rules in Mar. 79 Journal

SARTG 18-19 August 1979

CARTG 20-22 October 1979

WAEDC 10th-12th November 1979

If any of the above are in error please write to me or give me a call on the telephone. Thank you. SKIP.

CQ DAFG - CONTEST

Please note: Revised rules, effective from Jan. 1st 1979

GENERAL: The Deutsche Amateur-Fernschreib-Gruppe "DAFG" sponsors the 8th DAFG-SHORT-CONTEST 1979 and welcomes participation of all RTTY-Amateurs inside and outside Germany. There will be a SW- and a VHF-Contest. Both Contests will be scored separately. The Contest is split in 5 single-contests within the year. After closing the 5th single-contest, the winner of the year in each classification will be stated.

SCHEDULE:

SW:

1st part Saturday January	20th, 1979 1300-1600 GMT
2nd part Sunday March	18th, 1979 0800-1100 GMT
3rd part Saturday June	09th, 1979 1300-1600 GMT
4th part Sunday September	09th, 1979 0800-1100 GMT
5th part Saturday November	24th, 1979 1300-1600 GMT

VHF:

1st part Sunday January	21th, 1979 0700-1100 GMT
2nd part Saturday March	17th, 1979 1200-1600 GMT
3rd part Sunday June	10th, 1979 0700-1100 GMT
4th part Saturday September	08th, 1979 1200-1600 GMT
5th part Sunday November	25th, 1979 0700-1100 GMT

BANDS: Shortwave: 80 + 40 m VHF: 2m + 70cm

CONTEST CALL: CQ DAFG - CONTEST. After each QSO the station having called last keeps the QRG. The previous holder should make QSY. This QSY-rule is not (not) valid for the VHF-part!

EXCHANGE: SW: RST / QSO-number (start with 001) / Name / QTH

VHF: same as SW, in addition: QTH-locator.

SCORING: Each station may be worked once per band.

SW: Each complete QSO counts 1 point on 80 + 40 meters.

VHF: Each complete QSO counts at 2 meters per each 10 km's one point, at 70 cm's per each 10 km's distance 3 points. Each different prefix, per each band will be counted as a multiplier. Contacts via repeaters are not (not) valid.

FINAL SCORE: Total of QSO-points multiplied by total of multipliers.

CLASSIFICATIONS:

SW:

Class A: SW-stations above 200 watts input

Class B: SW-stations up to 200 watts input

Class C: SWL-stations

VHF:

Class D: VHF-stations

LOGS: must contain: SW: a) Call / Name and complete address of participant (use block letters, please)

b) Classification

c) GMT / Call, Name, QTH of Partnerstation / RST and QSO-number sent and received / Band used / number of prefixes

d) Final score (logs without final score will count as checklog)

VHF: a) to d) same as SW

e) QTH-locator sent and received

SWL: For points, multipliers and scoring confirm as above. The same station may be reported maximum 5 times. Instead of Message received Info, the SWL should report Call of partnerstation (wkd).

RESULTS: The results will be published in the news-bulletins of the DAFG, in RTTY-magazine, in the DARC-magazine and foreign courtesy publications.

DEADLINE: Your Log should be in the hands of the Contest-manager not later than 20 days after closing each single Contest. Each later incoming Log will count as a checklog only. All decisions are final.

CONTEST-MANAGER: Klaus K. Zielski DF 7 FB P.O. Box 1147 D - 6455 Erlensee 1 West Germany.

8th SARTG WORLD WIDE RTTY CONTEST 1978 RESULTS

Class A Single Operator

CALL	QSO's	Points	CALL	QSO's	Points	CALL	QSO'S	Points
I3FUE	287	298,540	ZS6AKO	88	23,490	W8TCO	10	900
IT9ZWS	251	247,845	VE7DTA	61	23,345	G4EDR	12	840
K3KD	214	214,825	W5HEZ	65	21,980	SM0LIB	11	735
F9XY	240	240,800	VE7DLX	64	20,020	PA0KFF	9	700
HB9AVK	212	233,225	DT3CF	74	19,865	JRAG	12	675
SM6GVA	246	232,815	F2PY	53	19,180	VK8HA	5	300
W3FV	199	217,350	JA2JHR	57	17,955	W8GKW	5	125
K0BJ	203	211,640	OZ2X	46	17,760			
SM6ASD	206	207,260	I1EPJ	61	17,030			
DT3YSO	181	182,700	LA7AJ	60	16,770	CLASS "B" MULTI-OPERATOR		
I7FKO	197	170,000	HB9HK	67	16,100	I5MYL	209	244,925
EA8IY	174	164,745	DM5VVL	51	16,050	DL0TS	196	183,150
I2OLW	188	151,585	G3HJC	40	15,840	LZ2KRR	197	182,150
K8NN	171	151,470	EA4XW	60	15,640	I1COB	180	153,655
DT2EDL	159	150,060	DM2DLE	73	15,120	G3UUP	165	152,800
DF2KU	182	147,060	DM5XNN/P	49	14,980	DM3CM	158	146,150
W9RY	172	146,160	SM7BGE	50	14,145	DK0CW	135	99,450
DL2XP	151	140,180	VK2SG	50	14,155	OH1AD	136	99,000
WA9BOW	158	136,000	WB5QBY	50	13,750	OH1AR	149	97,650
G3RED	170	133,835	G3RDG	51	13,200	OZ7SAC	106	67,925
SM4CNN	161	126,000	SM7MO	51	12,740	YO3KWA	124	60,720
SM5EIT	144	120,815	W0MT	41	11,375	HA5KEM	109	57,330
I2DML	138	107,730	OZ1BGQ	47	11,340	TF3SB	123	54,200
W4CQI	143	103,740	DL8WA	48	11,125	VE3OCU	87	33,635
I5HZZ	131	102,845	OK2BJT	37	9,625	OK1KWN	50	16,200
IS0RUH	143	100,920	EA6EQ	52	9,350	IM5LG	40	9,750
DK1BX	120	100,800	LA2LJ	34	9,020	SK6GX/6	22	3,000
DJ2YA	116	95,265	9M2CR	40	8,960			
DJ6QT	113	90,560	SM6BUV	43	8,925	SWL's		
OH2ZY	135	86,435	DK5GG	25	7,375	F. Rossi	229	218,550
K6WZ	108	78,080	K4YSB	30	7,290	OK1-1L857	208	209,700
WA6WGL	110	73,815	EA3AZX	37	7,110	Niendorf	215	206,640
I0LVA	107	72,300	K5EV	27	6,405	G8CDW	104	72,600
SM6AEN	107	68,685	JR2TZL	34	6,240	Wustner	154	70,265
OH6YI	151	66,400	DL10Y	28	6,175	DM-8987/K	93	53,805
JA7ML	100	58,500	DM4MF	57	6,000	DM-7111/A	96	46,560
CE3MA	90	54,530	3D6AD	35	5,200	OK2-21478	162	32,965
DJ2YE	75	50,740	DM2CHD	39	4,800	OK1-20677	103	32,640
YV5GU	78	48,530	WB2VTD	25	4,270	Schonwalder	101	16,540
LU3EQ	74	45,305	WB2WZX	24	4,125	DM-8747/7	20	3,280
W3KV	75	44,220	DM4SDA	25	3,675	DM-2814/M	16	1,920
YO2TS	83	40,500	LA8SA	29	3,240			
VE2QO	118	38,280	DZ8GA	21	3,000	Check logs..Many thanks to:		
IV3PVD	81	37,835	DM4VDA	18	2,960	K7GW, W6JOX, IS0ESS, DT2GRO,		
DL6WZ	74	35,070	TF3US	22	2,800	IS0YPW, I3RUF.....		
DT6AK	78	29,260	DJ1XT	14	1,485			
SM6CAL	71	26,250	DM3YF	16	1,400			
WA6CQW	61	24,840	DM2BCD	19	980			
			K8UFW	12	900			

21 CONT.

THE RTTY JOURNAL offers the RTTY Merit Award for single band WAC, the award is in the form of a certificate and is issued free upon presenting proof of contact to the QTH at the head of this column, WB6-CYA,. As of the end of 1978 the Award has been following Amateurs.

WAC 3.5MHZ

W1MX

WAC 7.0 MHZ

DLØTD

W1MX

WAC 14.0 MHZ

K3SWZ

WØMT

W5RYA

DJ8BT

SL5AR

DK4ZF

JH1TFE

I3-13-018

DJ1QT

W4ZLH

VP2MRW

F6ALL

K4YZV

W7JWI

SM6AEN

W1MX

W9OEQ

K6WZ

G3ZWW

DL8VX

W3EKT

WØJCO

PY2CYK

WB9LUK

WA6WGL

WB4TPU

K4GJW

DL8QP

I8YRK

G3YDR

I1PYS

LA2IJ

JA7ML

G3HJC

W8JMG

K1LPS

WB4VUP

W1GKJ

VE2QO

K4ZS

OHØNI

WAØYDJ/4

K4VDM

G4ALE

GW3IGG

K4JAFWA9AKT

W6JOX

JA4ONZ

BRS-18456

G3IIR

N3AI

I5HZZ

I5GZS

I20LW

I5KPK

SM5EIT

WA8CZ8

WA9BOW

B. Niendorf

K4RN

ISØESS

K5GH/W5KHP

HB9AVK

WB6CYA

I2WEG

WB2VTD

WA6CQW

K. Wustner

KØHSC

WAC 210 MHZ

WØMT

DJ8VX

SM6AEN

K6WZ

W3EKT

WA6WGL

W6JOX

W4YJ

I5WT

HB9AVK

SM5EIT

WAC 28.0MHZ

FG7XT

WA6WGL

DJ8BT

W1GKJ

W6JOX

HB9AVK

SM5EIT

WORKED ALL STATES

K3SWZ

W2PLQ

K4YZV

FG7XT

W1GKJ

W4CQI

WA8NGJ

W9OEQ

I8AA

DXCC Listing as of 1 Jan 1979

1. ON4BX
2. W3KV
3. I5KG
4. ON4CK
5. W5QCH
6. W8CQ
7. WA3IKK
8. DK3CU
9. W5EUN
10. G6JF
11. W2LFL
12. I5ROL
13. W4YG(K7BV)
14. W3DJZ
15. JA1ACB
16. K8YEK
17. I5WT
18. W1GKJ
19. W4CQI
20. DL8VX
21. K6WZ
22. W3EKT
23. W8JIN
24. W4EGY
25. I8AA
26. K3SWZ
27. OK1MP
28. W5VJP
29. K4YZV
30. K7BV
31. F6ALL
32. F5JA
33. HB9AVK

From the Publisher.


Hi gang.. lots of new news. First of all you will notethat George Hammond, WA6CQW has taken over Chuck, W6MNO's column. Chuck will be missed and I am sure that we all would like to thank him in person. Chuck has retired now and will be moving a-round more so you all never know when he will pop-upin your neck of the woods.

John Goheen III will be taking on some of the editors work. John usu-ally answers to the name of "Jay" around here as his father is also a John but John the elder just happens to be the guy I married recently. Jay has been in the Navy and retired recently with lots of electronic and printing experience. John(my guy) is retired from Scott Paper Company and now helps (?) me with the Journal.He answers most of the mail and puts the JOURNAL into the proper mail bags when it is time to mail the JOUR-NAL to you.

So hello to the new guys on the block... Take care and enjoy to the past Editor of Hits and Misses,Chuck. We all will miss you.

Hope tosee all of you in Dayton, April 27, 28, 29, 1979. RTTY-ers gather at the Imperial House North.

As ever,
Dee Crumpton-Goheen
Publisher

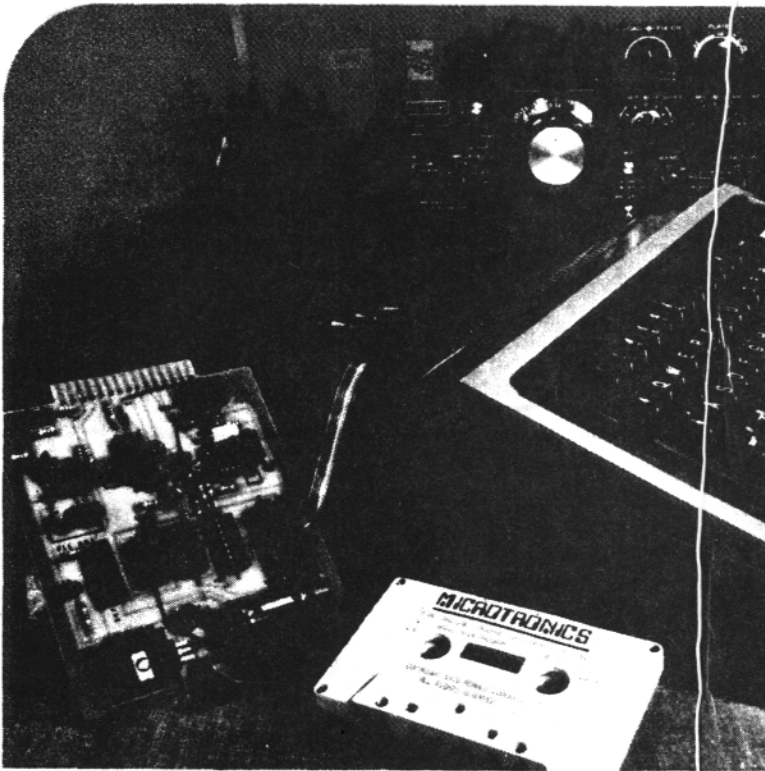


TRS-80 OWNERS

Send-Receive RTTY & CW

- Automatic send & receive: RTTY & CW
- Complete hardware and software package
- Connects to your TRS-80 User Port and the key/headphone jacks of your rig
- Ten message memories--255 char. each
- Keyboard buffer--allows typing ahead
- Uses built-in PLL or external TU
- Morse trainer--random 5 letter words
- Includes hardware, cassette & manual

\$99 KIT **\$129** WIRED

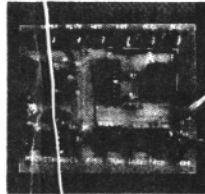


PET version available,
\$69.95 KIT
\$99.95 WIRED

MICROTRONICS

Write or call for detailed brochure

California residents add 6% tax

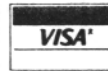P.O. Box 747 (R) Keyes, CA 95328 / (209) 634-8888 / (667-2888



INFO-TECH M-300

THE SUPER KEYBOARD THAT GENERATES:

Morse 4 to 125 WPM
 ASCII 110 & 300 Baud
 RTTY 4 speeds, 2 shifts using built in function generator
 AFSK. Built in QUICK BROWN FOX. Built in RY generator. User programmable CWID. Auto CR/LF.
 700 character running buffer and 10 recallable message memories of 120 characters each and much more. Price \$450.00 F.O.B. factory




Mastercharge & Visa accepted
 For more information write:
 Info-Tech, Inc.
 2349 Weldon Parkway
 St. Louis, Missouri 63141






Data Processing Quiz

Digital circuits are becoming important in the control circuits of ham radios: in keyers, in channel selection switching, in repeater controllers, in memory devices and others. The output is simply a change in the D.C. level of the output connection, usually from a near-zero level, called "Low" or "0", to a level of a few volts, called "High" or "1". There are no in-between levels. Outputs are of small current but can drive other logic, diodes or transistors, which can supply "muscle current" of high ampereage.

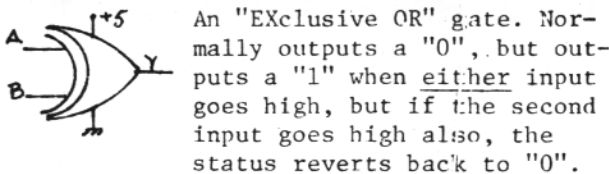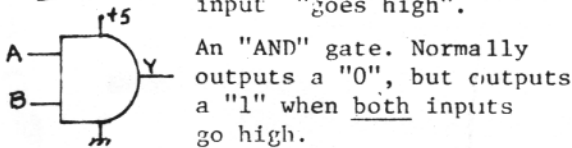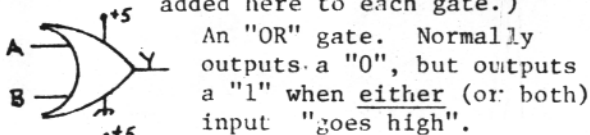Symbols have been developed to show "gates", a place where a comparison is made to either output High or output Low. (TTL circuits operate from +5VDC, added here to each gate.)



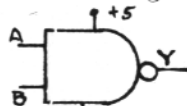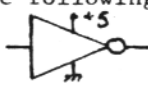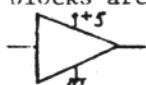
Other equally important logic building blocks are the following:



Digital logic circuits are designed to handle the "and" and "or" relationships that exist not only in mathematical processes but in everyday life as well.


Because these circuits are simple and very low powered, they can be small and packaged together. Here are 4 2-input AND gates in a "Quad" package.

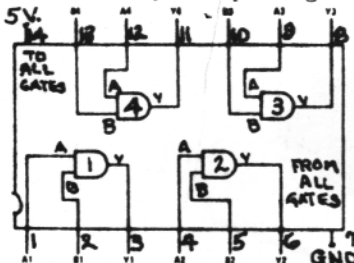7408
Quad 2-input AND Gates.
Size: .75 x .25 x .130 in.



Actually the package contains 12 diodes, 24 transistors and 20 resistors. And it's among the simple ones!

---by K6KH

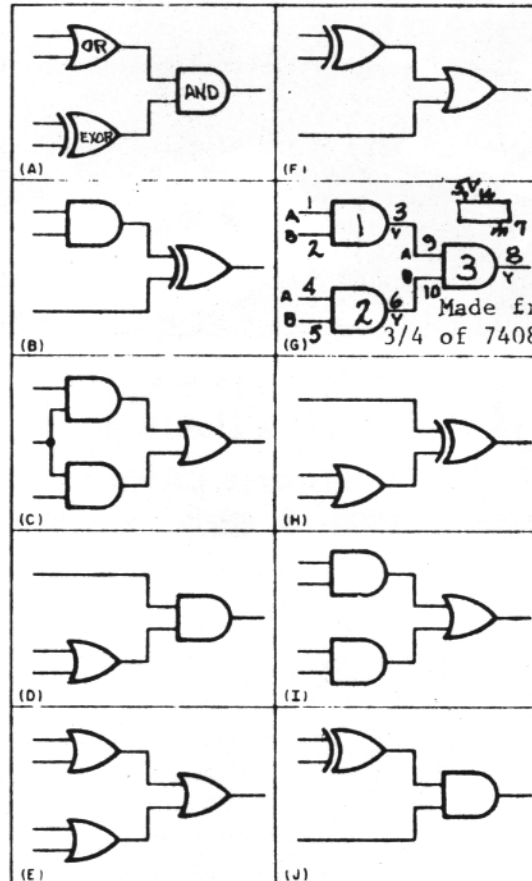

Situation Figure

- 1.
- 2.
- 3.
- 4.
- 5.
- 6.
- 7.
- 8.
- 9.
- 10.


Digital logic circuits are designed to handle the "and" and "or" relationships that exist not only in mathematical processes but in everyday life as well.

To test your ability at understanding logic, see if you can match the following common situations (1 to 10) with the analogous circuits (A to J).

- 1 To win a prize you must send in a coupon and also get at least one of the question is right.
- 2 Today's luncheon special consists of a ham sandwich with either soup or a salad, but not both.
- 3 You can paint the walls blue or pink but paint the ceiling white, even if you don't do the walls.
- 4 A pair of Jacks or a pair of Queens will win the hand.
- 5 They will rent the apartment to a couple or a single person, but not to both.
- 6 On this TV set, you can get the sound and picture separately or together on channel 5, but the sound only on channel 8.
- 7 To get in, you must have \$4.00 and either, a discount card or come up with another dollar.
- 8 You must attend at least one morning or afternoon session of either day of the conference.
- 9 If you take a course in Law or Sociology, or both, you must also take one in either English or History, but not both.
- 10 You can play doubles at tennis there; but if a player on either team fails to show up, the game is called off.



VHF RTTY NEWS

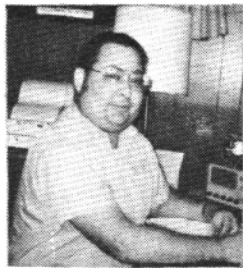

Arny Gamson, K6PXA, 8034 Gentry


N. Hollywood, CA 91605

RC lowpass filter (R17, R19, C11) but it leaves a lot of room for improvement. The circuit below is adapted from the ST-6 design. The input, output and power connections refer to figure 9 of the second edition.

425 shift — The modification is very easy. Simply remove C2a (0.033 pF). C2 (9.1 pF) in parallel with L2 results in a calculated resonance within 4 Hz of the desired 1700 Hz. It is appreciated that such a simple step cannot produce an ideally balanced discrimination but because of its simplicity, possibly including a single pole switch to make the TU "dual shift," makes the modification worthwhile.

RTTY bartg newsletter journal of the British Amateur radio teleprinter group

Of all the improvements that can be made to a simple TU, inclusion of a good post detector lowpass filter is likely to give the most marked difference in copy of poor signals. The theory is that as a 45 Baud RTTY signal transmits all its information in the spectrum DC to 22 Hz a lowpass filter, of cut-off frequency say 25 Hz, wired immediately after the detectors will not remove any wanted signalling information but will attenuate unwanted higher frequency components i.e. noise, QRM etc. The basic ST-5 TU does contain a simple

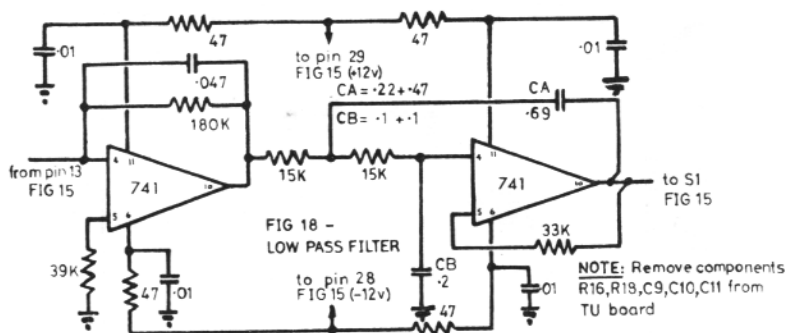

The following are the most used manuals for the 28 ASR & KSR TTY;

BULLETIN NUMBER	CONTENTS	PRICE
217B	28KSR ADJUSTMENTS AND LUBRICATION	\$15.40
235B	28TD ADJUSTMENTS AND LUBRICATION	6.30
247B	28 REPERF ADJ. & LUB.	12.70
250B	28ASR KBD BASE & PERF ADJ. & LUB.	11.10
295B	MOTOR UNITS, COMPLETE MANUAL	4.75
1149B	28KSR PARTS	14.70
1161B	28TD PARTS	4.50
1167B	28 REPERFORATOR PARTS	8.45
1169B	28ASR PARTS	14.20

If you order the whole "shootin' match," it is advisable to ask for UPS COD Shipment. Order from:

Teletype Corporation
Bulletin Order Department
5555 Touhy Avenue
Skokie, IL 60076
Attn: Frank Sandy



A.D.M. Communications, Inc.

Teletype & Communications Equipment


Doug Mathena

(714) 747-0374


1322 Industrial Ave. Escondido, California 92025

SALES and SERVICE **New & Used Teletype Machines**

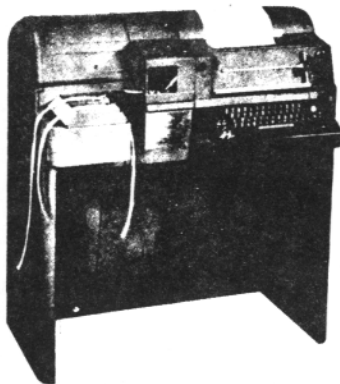COMPLETE REPAIR ■ RE-BUILDING
PARTS ■ PAPER ■ MOD. KITS
REPERFS ■ T.D.'s ■ RE-WINDERS



Model 28ASR

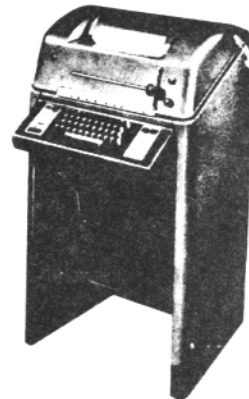

Model 28KSR


WA6PMA

DOUG

HITS & MISSES

George Hammon WA6CQW
14215 Pecan Park Lane SP 73
El Cajon, CA 92021

FROM
THE
MAILBAG

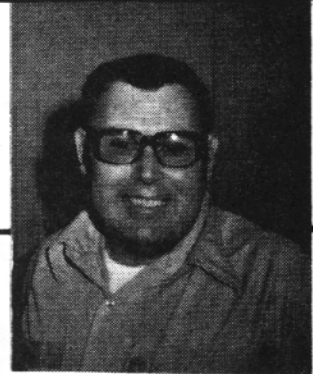

With the beginning of this issue I will be writing the HITS and MISSES column. It will be my pledge to bring you, the readers, an informative column. But this requires INPUT, so let me hear from you. "Happiness is a full mailbag."

Being the new kid on the block, let me introduce myself. . . . I was born 47 years ago in St. Louis, Missouri and moved to San Diego in 1947. My XYL's name is Jeanne.

I have a degree in criminology and currently hold the position of forgery fraud investigator in the San Diego Police Department. In 1958 I earned my ham license and in 1965 I became interested in RTTY and have been hooked ever since.

At present, I use the Kenwood TS820S along with a Swan Tribander beam, Info-Tech TU M200 and M300 keyboard with video display. I generally use low power (40 watts) and try to participate in most contests. I have numerous other pieces of RTTY equipment such as; HAL ST5, TU Swan linear, etc. . . I won't bore you with a list of give the XYL a check list on where the money goes.

I was very happy to hear that Arny, K6PXA is on the mend. Hopefully he will soon be able to make the long drive to the San Diego Teleprinters Society meetings again. Get well, Arny and come see us.

Speaking of the San Diego Teleprinters Society, the new president for 1979 is Bob Smith, WB6ODR. The Teleprinters conduct meetings each fourth Tuesday of the month at the Bonanza Steak House, 8105 Clairemont Mesa Blvd, San Diego.


The first week of the new year the XYL and I drove over to Las Vegas, Nevada to attend the midwinter Consumer Electronics Show. We really enjoyed it. I chatted with many hams and stopped by the ARRL booth to put in a pitch for RTTY. I spoke with Leonard Norman about the chance of the SAROC ham convention starting up again and was left with an optimistic opinion that it well may. Also, I noticed that Hy Gain and Nutronics were in attendance and the size of the show was fantastic. The range of electronics devices on display would keep you drooling for days. The show program listed over 300 exhibitors. I spent over half an hour trying to find a parking place.

Dee, our publisher, is looking for articles, not only for the Journal but also for

the RTTY Handbook. So sharpen your pencils and submit your articles. In the last few weeks I received some nice notes from many of the RTTY club stations in Europe. Many included photos along with their QSL cards. So let me hear from you.

So long for now, George.

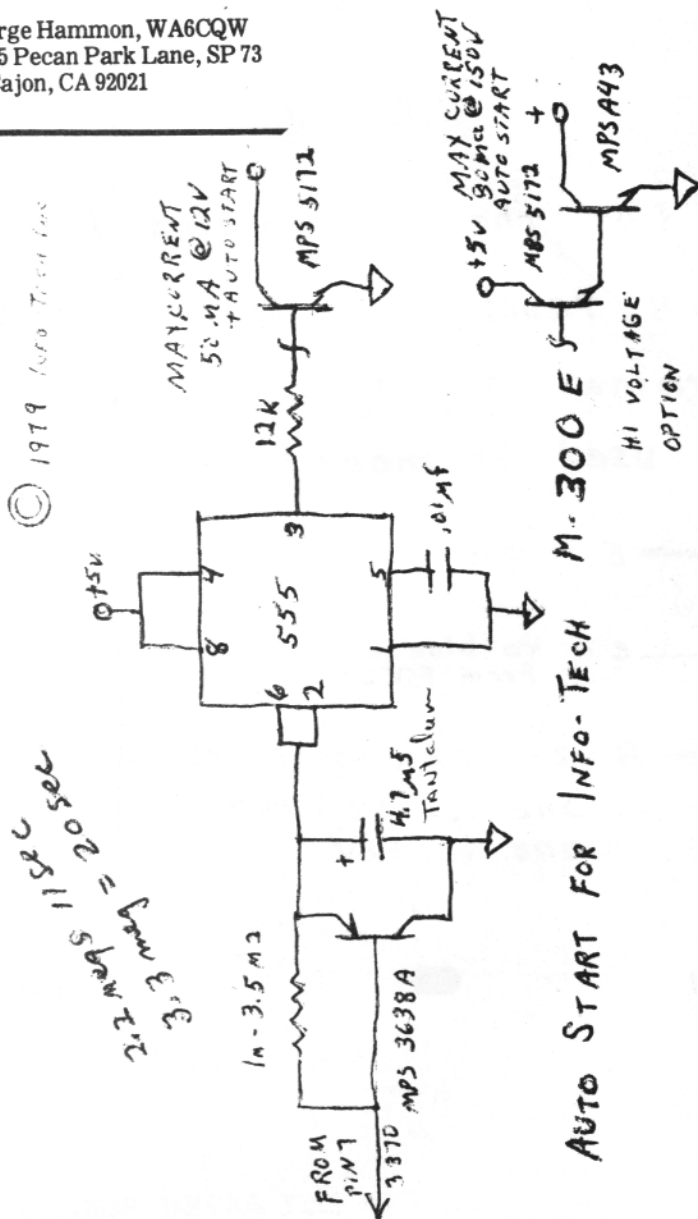
George Hammon, WA6CQW
14215 Pecan Park Lane, SP 73
El Cajon, CA 92021





ADDITIONAL SCHEMATIC FOR INFO-TECH M-300 TRI-MODE KEYBOARD.

INVERTER FOR YAESU FT901DM

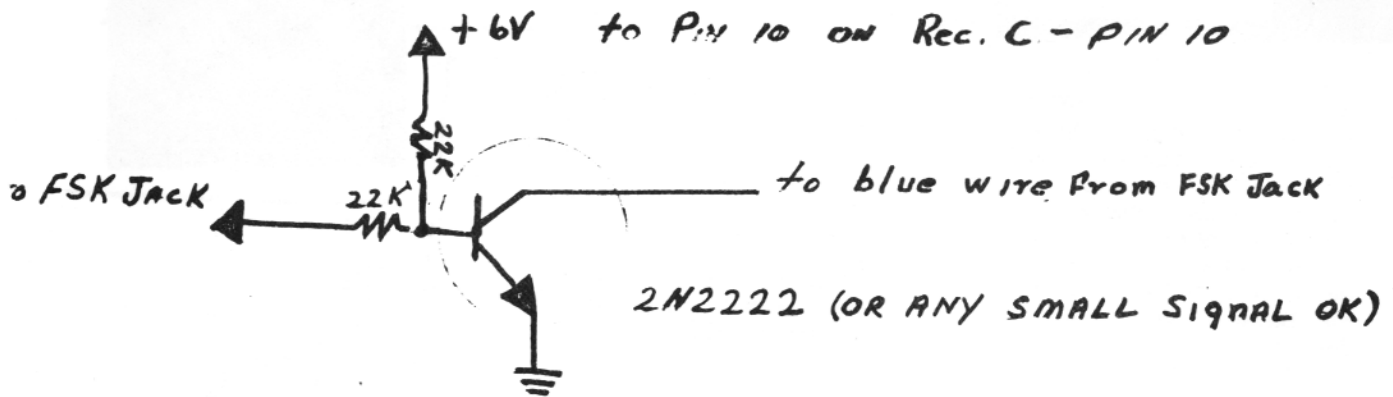PETE HARRIS, WB1CRG
 18 VERA ROAD
 COVENTRY, RI 02816



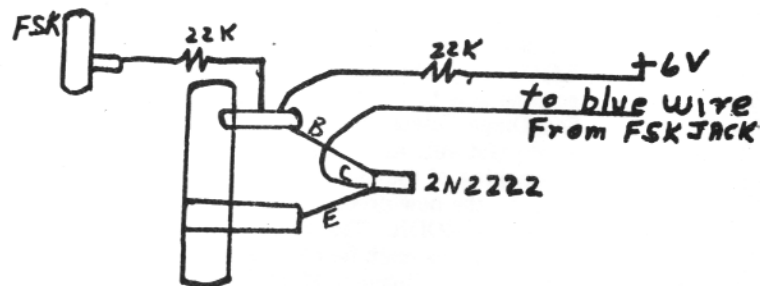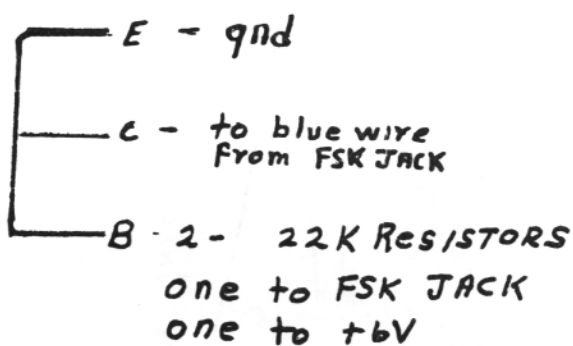Cut the wire going to the FSK Jack on the back panel and insert the Above. There is a terminal strip below the FSK Jack which can be used to mount the components



PETE WB1CRG

GET YOUR RTTY JOURNAL HANDBOOK NOW...ONLY \$4.50

BRUCE J. FRAHM KØBU
 P.O. Dr. for DX
 COLBY, KANSAS 67701

M/V YANKEE TRADER'S 1977 ROUND THE WORLD CRUISE ITINERARY
 by Rowland S. Wilson

Cruise Day	Time Kept Off GMT	Port No.	Port	Time & Date of Arrival	Days in Port	Port	Time & Date of Departure	Naut. Miles	Days at Sea	Av. Spd. (kts)	Total Naut. Miles
1	-5	1	-Freeport, Bahamas	0905	2.06	-Freeport, Bahamas	1715	572	2.68	8.89	572
4-6	-5	2	Cap Haitien, Haiti	1008	0.25	Cap Haitien, Haiti	1108	189	0.96	8.21	761
7	-5	3	Port Au Prince, Haiti	0730	9.38	Port Au Prince, Haiti	1602	980	5.64	7.23	1741
13-22	-4	4	Fort DE France, Martinique	0620	0.53	Fort DE France, Martinique	1910	444	1.74	10.65	1853
23	-4	5	Admiralty Bay, Bequia	1250	2.08	Admiralty Bay, Bequia	1255	752	3.18	9.86	2297
25-27	-5	6	Kralendyk, Bonaire	1710	0.44	Kralendyk, Bonaire	0345	50	0.42	4.96	3049
30-33	-5	7	Cristobal, PCZ	1350	4.14	Cristobal, PCZ	1715	657	3.72	7.36	3099
33-37	-5	8	Balboa, PCZ	1125	6.79	Balboa, PCZ	0616	2419	9.10	11.07	3893
41-48	-5	9	-Guayaquil, Ecuador	0837	2.41	-Easter Island	1841	1139	4.57	10.37	6175
57-59	-6	10	-Easter Island	0828	1.43	-Pitcairn Island <i>may stay 3-4 days this year</i>	1840	1205	5.56	9.03	7314
64-65	-8½	11	Papeete, Tahiti	0806	5.63	Papeete, Tahiti	2320	95	0.43	9.16	8518
71-76	-10	12	Port de Fare, Huohine	0942	1.10	Port de Fare, Huohine	1212	25	0.11	9.15	8614
77-78	-10	13	Uturoa, Raiatea	1456	1.64	Uturoa, Raiatea	0610	30	0.18	6.95	8639
80-84	-10	14	Vaitape, Bora Bora	1030	3.85	Vaitape, Bora Bora	0700	619	2.97	8.52	8669
87	-10½	15	Avarua, Rarotonga, Cook Island	0630	0.87	Avarua, Rarotonga, Cook Island	1750	757	4.07	8.80	9288
91-93	-11	16	-Pago Pago, Tutuila, Am. Samoa	0805	1.89	-Pago Pago, Tutuila, Am. Samoa	0625	83	0.35	9.76	10045
93-96	-11	17	-Upolu Is., Apia Harbor, W. Samoa	1455	2.63	-Upolu Is., Apia Harbor, W. Samoa	0602	663	2.72	10.15	10128
	-12/+12	18	International Date Line	2400		International Date Line	0000	608			
99-104	+12	19	-Suva, Fiji	0019	5.70	-Suva, Fiji	1700	70	2.64	9.58	10791
107-109	+11	20	Vila, Efate, New Hebrides	0725	1.81	Vila, Efate, New Hebrides	0250	28	0.32	9.00	11399
109	+11	21	Sesaki, Anchorage, Emae(Mai) Is.	1036	0.19	Sesaki, Anchorage, Emae(Mai) Is.	1505	92	0.19	6.00	11469
109-110	+11	22	Foreland Anchorage, Ise Epi	1807	0.25	Foreland Anchorage, Ise Epi	0001	652	0.36	10.70	11497
110-111	+11	23	Santo, Espiritu Santu	0803	1.34	Santo, Espiritu Santu	1656	92	2.88	9.47	11589
114-116	+11	24	Honiara, Guadalcanal, Solomon Is.	1407	2.09	Honiara, Guadalcanal, Solomon Is.	1618	936	4.10	9.52	12241
120-127	+10	25	-Port Mortsby, Papua New Guinea	1835	6.93	-Port Mortsby, Papua New Guinea	1700	243	1.02	9.95	13177
128-129	+10	26	Dalrymple Islet	1725	0.59	Dalrymple Islet	0740	834	3.58	9.69	13420
132-133	+9½	27A	Fannie Bay	2009	0.52	Fannie Bay	0840	7	0.05	5.36	14254
133-136	+9½	27B	Port Darwin, Australia	0958	3.35	Port Darwin, Australia	1815	976	4.02	10.11	14261
140-141	+8	28A	Harbor Entrance, Benaos, Bali	1742	0.68	Harbor Entrance, Benaos, Bali	0956	5	0.02	10.00	15237
141-148	+8/+7	28B	Benaos Port, Bali	1025	7.24	Benaos Port, Bali	1605	1035	4.25	10.24	15242
152-153	+7½	29A	Eastern Roads, Singapore	1000	0.49	Eastern Roads, Singapore	0944	1	0.03	1.60	16277
153-168	+7½	29B	Inner Harbor, Singapore	1022	15.22	Inner Harbor, Singapore	1540	397	1.71	9.70	16278
170-173	+7½	30	Penang	1040	3.18	Penang	1505	1312	6.11	8.94	16675

also possibly HS r
 901 during this time

M/V YANKEE TRADER'S 1977 ROUND THE WORLD CRUISE ITINERARY
by Rowland S. Wilson

Cruise Day	Time Kept Off GMT	Port No.	Time of Arrival	Time & Date of Arrival	Days in Port	Port	Time of Departure	Time & Date of Departure	Naut. Miles	To Next Port		
										Days at Sea	Av. Spd. (Kts)	Total Naut. Miles
179-189	+5 1/4	31	1550	13 Aug	9.98	Colombo, Sri Lanka	1540	23 Aug	411	2.06	8.25	17987
191-193	+5	32	1530	25 Aug	2.03	- Malé, Maldives Ja.	1615	27 Aug	1288	5.99	8.69	18398
199-204	+4	33	1455	2 Sep	5.11	Mahé, Seychelles	1737	7 Sep	951	4.64	8.55	19686
209-218	+3	34	0850	12 Sep	9.11	- Mombasa, Kenya	1505	21 Sep	565	3.01	7.83	20637
221-222	+3	35	1515	24 Sep	1.21	Mutsamudu, Agulhas Islands	2010	25 Sep	85	.48	7.34	21202
223-224	+3	36	0745	26 Sep	0.90	Zanzibar (Dzaodzi) Is Comares	0520	27 Sep	741	3.45	8.95	21287
227-229	+3	37	1605	30 Sep	1.73	Tulear, Madagascar	0630	2 Oct	1574	7.14	9.16	22029
236-248	+2	38	0920	9 Oct	12.20	Cape Town, So. Africa	1402	21 Oct	1705	7.71	9.20	23603
256-257	0	39	0605	29 Oct	1.49	- Jamestown, St. Helena	1750	30 Oct	1770	7.90	9.34	25308
265-272	-3	40	1320	7 Nov	6.76	Recife, Brazil	0740	14 Nov	2096	8.38	10.42	27078
280-284	-4	41	1547	22 Nov	3.93	Port of Spain, Trinidad	1402	26 Nov	103	0.56	7.73	29174
285-287	-4	42	0322	27 Nov	2.03	St. Georges Harbor, Grenada	0405	29 Nov	37	0.21	7.40	29277
287-288	-4	43	0905	29 Nov	0.63	Hillsboro, Carriacou	0015	30 Nov	43	0.26	6.88	29314
288	-4	44	0630	30 Nov	0.46	Kingstown Bay, St. Vincent	1730	30 Nov	132	0.65	8.50	29357
289	-4	45	0900	1 Dec	0.42	Roseau, Dominica	1905	1 Dec	44	0.23	8.18	29489
290	-4	R/V	0030	2 Dec	0.05	Les Salines, St. Pierre & Miquelon	0140	2 Dec	73	0.39	7.85	29533
290	-4	46	1100	2 Dec	0.53	English Harbor, Antigua	2350	2 Dec	88	0.40	9.16	29606
291-292	-4	47	0928	3 Dec	1.31	Gustavia, St. Barthelemy	1650	4 Dec	14	0.07	7.77	29694
292-294	-4	48	1838	4 Dec	1.74	Philipsburg St. Maartens	1220	6 Dec	28	0.14	8.24	29708
294	-4	49	1545	6 Dec	0.36	Saba	1935	6 Dec	97	0.50	8.05	29736
295	-4	50	0738	7 Dec	0.40	- Port Purcell, Road Harbor	1708	7 Dec	12	0.06	8.18	29833
295-296	-4	51A	1828	7 Dec	0.60	- St. Thomas Bay, Virgin Gorda	0852	8 Dec	1	0.01	3.00	29845
296	-4	51B	0912	8 Dec	0.23	- The Baths, Virgin Gorda	1445	8 Dec	792	3.97	8.10	29846
300-302	-5	52	1403	12 Dec.	1.43	- Nassau, Bahamas	0035	14 Dec	121	0.56	9.01	30638
302	-5	53	1400	14 Dec	-	- Freeport Harbor, Bahamas	-	-	-	-	-	30759

163 days in port (30759 n.m. at 9.22 knots)

139 days underway

FROM THE COMPANY WITH A LONG LINE OF RTTY FIRSTS

RVD-1002
1st RTTY
Video Generator



1971


1972



DKB2010
1st RTTY & MORSE
Keyboard

1973

RVD-1005
Improved RTTY
Video Generator

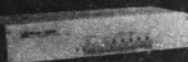

1974

1975



ST6000
High-performance
RTTY Demodulator

DS3000 KSR Version 2
1st Microprocessor
Controlled Amateur Equipment
with Editing for Baudot & ASCII




1976

1977

1978

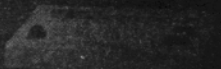DS3000 KSR Version 3
1st 3-mode Amateur Send-Receive Terminal
for Baudot, ASCII, and MORSE



1979

ST5000
Low-cost, Big-performance
RTTY Demodulator




AND NOW...

DS3100 ASR

The **FIRST** Automatic Send-Receive Electronic Terminal for Baudot, ASCII, and MORSE

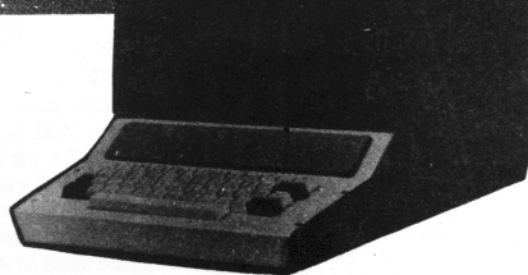- Type and edit your message while receiving
- 200 line storage
- Non-volatile and programmable HERE-IS
- Internal real-time clock
- WRU answer-back
- 24 line screen
- RTTY and CW ID
- Upper and lower case ASCII



\$1995.00
Call or write
for complete
new catalog



HAL COMMUNICATIONS CORP.
Box 365
Urbana, Illinois 61801
217-367-7373

In Europe contact:
Richter & Co.; Hannover
I.E.C. Interelco; Bissone

Classified Ads

30 words \$2.00. Additional Words 4 c ea.

Cash with Copy - Deadline 1st of Month.

THE DOVETRON SSD-100 solid state cross display replaces the conventional CRT and associated high voltage power supplies as the tuning indicator in the MPC-Series RTTY terminal units.

In addition to "instant-on" operation and a predicted reliability in excess of 100,000 hours, the solid state display out-performs the original CRT in every instance.

The absence (or deactivation) of the high voltage supplies and the resultant decrease in heat generation increases the MTBF (Mean Time Before Failure) of the terminal unit more than 10 times.

The display itself consists of high intensity (4 millicandelas), red, rectangular LEDs (Light Emitting Diodes) arranged in the traditional cross pattern and operated in a baragraph mode. The two LEDs that form the apex of the cross are tied into the terminal unit's logic in such a way that they extinguish if the TU is improperly tuned to the incoming tones, or if the incoming signal is up-side down in respect to the "sense" of the terminal unit.

A separate LED in the upper left quadrant of the cross display monitors the two input channels and flashes in the presence of time or frequency dispersive multipath distortion, indicating that the MULTIPATH CORRECTOR should be turned on.

Separate LEDs in two other quadrants monitor the status of the internal loop, the Signal Loss circuit and the Send/Receive mode of the terminal unit, making the SSD-100 a convenient display center of the various functions. A light sensitive photocell in the fourth quadrant monitors the ambient light conditions at the operating location and automatically adjusts the display's light output. Under normal conditions, the SSD-100 may be read comfortably from 75 feet.

The new front bezel contains an anti-glare, optical filter and provides 30% more viewing area than the original CRT bezel.

A retrofit kit (SSD-100K) is available to update existing CRT-equipped terminal units in the field. Your inquiry will bring complete details by return mail. DOVETRON, 627 Fremont Avenue, (PO Box 267), South Pasadena, California 91030.

NEWS-NEWS-NEWS-Amateur Radio's Newspaper, "Worldradio". Trial subscription - Two issues for one dollar. "Worldradio", 2509-F Donner Way, Sacramento, California 95818.

NS-1A PLL Demodulator W/T \$26.95 ppd. Complete kit \$19.95 ppd. SASE for info. Nat Stinnette Electronics, Tavares, FL 32778.

Bandpass active filter 2125/2295 Hz. Easily tuned. Requires +12v. Complete kit \$11.95, W/T \$16.95 ppd. Nat Stinnette Electronics, Tavares, FL 32778.

YOU NEED Information on Commercial RTTY Stations? News Agencies, Telex, Weather..on shortwave? I have up-to-date frequency, callsign, schedule, code lists. Write for details. Joerg Klingentuss, Goethestrasse 14, D-7400, Tübingen 1, West Germany.

TELEPRINTER parts, manuals, gears, ribbons, paper, tape, converters; toneroids. SASE for list. Wanted: TT, KL, parts, 2BP1 etc., tubes. Typetronics, Box 8873, Ft. Lauderdale, FL 33310 WAN7F-N4TT.

HELP need information on wiring of 28ASR also schematic for the ST-5 or where one is available cheap. K80X0

CRYSTAL CONTROLLED XB-6 CLOCK BOARDS FOR THE UT-4. SINGLE SIDED PC BOARD HAS PROVISIONS FOR TWO CLOCKS FROM ONE CRYSTAL. MAY ALSO BE USED FOR NUDATA/DAYTAPRO UT4B BOARDS. BOARD SIZE 4½ x 6½ INCHES. PRICE \$8.95 COMPLETE KIT \$26.95. DAYTAPRO ELECTRONICS, (FORMERLY NUDATA ELECTRONICS), 3029 N. WILSHIRE LN., ARLINGTON HTS., IL 60004.

HOME REPERF FOR MODEL 28. 3 SPEED 60-75-100 WPM. WITH PRINTING REPERF. 150.00 INCLUDING SHIPPING. MODEL 28 ASR COMPLETE 275.00 PICK-UP ONLY. MODEL 33 ASR 385.00 PICK-UP ONLY. MODEL 33 KSR 225.00 PICK-UP ONLY. MODEL 28 KSR 135.00 PICK-UP ONLY. WANTED GOOD MODEL 12 FOR MY COLLECTION. M. WEINSCHENKER K3DPJ 12690 RTE 30 N. HUNTINGDON, PA. 15642. PHONE 412-863-7006 AFTER 6 PM.

6800 MICROPROCESSOR OWNERS - RTTY operating software for SWTPC or similar processors. Transmit Baudot or Morse and receive Baudot Code. Written for on the air use - keyboard selection of pre-loaded messages or CW ID. Can also be used as buffered CW keyboard with keyboard speed control. For more info and price send brief description of your system to K9AR, 742 So. Vail Ave., Arlington Hts., ILL. 6005.

The DOVETRON Binary Bit Processor (BBP-100) provides high-performance axis-restoration in the TEMPEST Model MPC-1000T and BASEBAND terminal units. This plug-in assembly is now available as a retrofit kit (BBP-100K) and may be easily added to existing MPC Series terminal units. In addition to Selectable Bandwidth and Automatic Multipath Correction, the BBP-100 has shown error rate reductions on weak and noisy signals in excess of 30 times. Your inquiry will bring full details by return mail. BBP-100K: \$145 postpaid. DOVETRON, 627 Fremont Ave., South Pasadena, CA., 91030.

The DOVETRON TBA-1000 Baudot-ASCII Code Translator is designed to interface Baudot and ASCII circuits. I/O may be low level polar (EIA RS232C or MIL 188C) or high level neutral (active or passive). Parallel ASCII is also available. A pre-loadable 192 character buffer prevents character over-runs when down-converting baud rates. ASCII Control characters may be used to command peripheral equipment and functions. Features such as Unshift/Space, LTRS Only, Blank Diddle, Variable Character Rate, LED Memory Status Indicators and TD Inhibit are standard. Baudot speeds of 45, 50, 57 and 75 bauds are front panel selectable. ASCII baud rates of 110, 150, 300, 600, 1200, 2400, 4800 and 9600 bauds are internally selectable via a BCD coded DIP switch. All baud rates are crystal controlled and programming instructions are etched on the PC board. The 3.5" x 9.0" x 17.0" package is self-contained and available as a table top or rack mount unit. Power requirements are 115/230 VAC, 40-400 Hz, 10 watts. A bypass option is available. Amateur Net: \$295.00 FOB. DOVETRON, 627 Fremont Avenue, South Pasadena, CA., 91030.

WHAT! THE ST-5 improved? You bet! The MEG-1 RTTY Demodulator is designed to be built by the beginner, modular, and easy to work on. Curious? For information and prices write to the Midnight Engineering Group, PO Box 349, Galesburg, IL 61401.

PRINTED CIRCUIT Board drill bits! You can now get carbide printed circuit board drill bits for a reasonable price. 1/8" shank, approximately 1" long. Four sizes available: .047" (approx. #56 drill), .043" (#57), .033" (#66), and .030" (approx. #68-69). \$1.25 each, includes shipping, Minimum Order Is Two Drill Bits. Illinois residents add 5% sales tax. Midnight Engineering Group P.O. Box 349, Galesburg, IL 61401.

ELECTRONIC KEYBOARD CABINETS. Six sizes available. Depth 8.4 in. Height 3 in. WIDTH 14 in. \$15.20, WIDTH 17 in. \$18.35, WIDTH 20 in. \$19.25. Depth 11.4 in. Height 3 in. WIDTH 14 in. \$16.50 WIDTH 17 in. \$18.80 WIDTH 20 in. \$20.75. **ALUM TOP AND BASE.** Shipping included in prices. Blue base with choice of black or white top. 10 Minute timer kit, Variable 1-20 minute \$8.95 Kit. Board Alone \$3.95

Daytapro Electronics, (formerly Nudata Electronics) 3029 WILSHIRE LN. ARLINGTON HTS, IL 60004

TU LOOP SUPPLY BOARD. Contains all necessary for +12 -12 low voltage supply with provisions for high voltage loop supply. Similar to that of ST-5. Ideal for most TU'S including DT500 and DT600 units. \$5.95 Per board plus .90 for shipping. Daytapro Electronics, (formerly NuData Electronics), 3029 Wilshire LN. Arlington, Hts., IL 60004.

RTTY ID GENERATOR. Accepts 5 or 12 volt supplies, 31 characters available, please include letters, figures, spaces etc. Your preprogrammed answer-back must be supplied with order. **EXAMPLE:** DE K9WRL NEIL ARL HTS ILL. Board same size as ST-6 boards \$34.99 Kit. Board Alone \$8.50. 5v Power supply for above \$11.95 **DAYTAPRO ELECTRONICS (FORMERLY NUDATA ELECTRONICS),** 3029 Wilshire Ln., Arlington Hts. IL 60004.

NEW CW ID UNIT. Includes many extras, on board interface for FSK and AFSK plus H.V. Interface, 10 Minute timer, variable speed 5-24 WPM, ON BOARD 7805 allows 5 or 12 volt use. \$37.90 kit. **MINI VERSION OV ABOVE, ID only with 7805 Regulator \$21.95 Kit. BOARD ALONE** (same for both units \$9.45. Power supply for above 5V at 1 Amp \$11.95 Kit. Daytapro electronics, (Formerly NuData Electronics), 3029 Wilshire Ln., Arlington Hts. IL 60004.

UT-4 KITS NOW AVAILABLE. Enough components to fill board. All necessary logic, resistors, diodes, transistors and capacitors. Complete documentation. Commercially made boards. Price \$109.95. **UT-4B BOARD** alone \$17.95 with documentation. Special mini parts package for **UT-4 BOARD** includes resistors capacitors, diodes and transistors. Price \$8.95. **M4D POWER SUPPLY** for above. Kit, \$31.95. Add \$1.00 for shipping. Daytapro Electronics, Formerly NuData Electronics, 3029 Wilshire Ln., Arlington Heights, IL 60004.

Ham Radio Magazine - The no-nonsense state-of-the-art technical magazine. Dozens of exciting projects and an emphasis on quality unmatched by any other radio magazine. Subscribe now and see for yourself. 1 year. \$12.00. 2 years \$22.00 and three years. \$30.00. Ham Radio Magazine, Greenville, NH 03048.

TELETYPE EQUIPMENT AND SUPPLIES. Model 28 RO, KSR, ASR AND TAPE equipment on hand and ready to go. Some Model 14 equipment available also. Most 14, 15, 19, 28 parts and assemblies on hand. **WANTED:** Gears for all Teletype Corp machines especially 60 speed for Model 28's. Also want Model 15 KSR AND RO's from local region. P. Andersen 115 Boyken Rochester, Michigan 48063 313/652-3060.

(70) TTY Solid State Keyboards with Baudot Output. Made By C.P. CLARE for Texas Inst. All units have never been on line. **PARRELL Output & Double shot keytops.** These units are first class. \$26.00 pp R.C. JOHNSON, E. 16109 LONGFELLOW, SPOKANE, WASH. 99216

TELETYPE SUPPLIES, Technical manuals, equipment. 11/16" and 7/8" perforator tape. Page paper. New ribbons. Teletype Corp. maintenance manuals. Let me know what you need. Send 75 cents postage for 3 current catalogs. **JIM COOPER, W2JC/W2BVE, Box 73, PARAMUS, NJ 07652.**

HAL-DS-3000 KSR FOR SALE: CRT Display, ASCII and Baudot. All manuals included. Mint Condition. 4 months old. Must sell, need money. Phone 1-416-281-9454, Bill VE3KDM, 36 Keeler Blvd., Scarborough Ontario. M1E-4KS.

TELETYPE TD paper 11/16 oiled ans yellow. Carton 10 \$3.00 wt. 13 lbs. Carton 40 \$10. wt. 47 lbs **ADD UPS wt. Harmon, 5628 10th Ave., S. Birmingham, AL 35222.**

KLIENSCHMIDT TD paper. 7/8" oiled and yellow. Carton of 8 \$3.75, wt 13, 7/8" carton of 32 \$12.00 wt. 47 lbs. **ADD UPS wt. HARMON, 5628 10th Ave., S. Birmingham AL 35222.**

COMPUTER HEATH H-8, 16K RAM, H8-5 serial-cassette I/O, H-S video terminal, documentation and software. \$1,200, W. Serp, 4027 Harvey Ave., Western Springs, IL 60558 (312)246-7856.

NS-1A PLL Demodulator W/T \$26.95 ppd. Complete kit \$19.95 ppd. SASE for info. Nat Stinnette Electronics, Tavares, FL 32778.

BANDPASS ACTIVE filter 2125/2295 Hz. Easily tuned. Requires + 12 v. Complete kit \$11.95, W/T \$16.95 ppd. Nat Stinnette Electronics, Tavares, FL 32778.

SELL: TEST sets T S-2/T G (Teletype) sends normal or distorted signals. (60-100 speed), (110/120 VAC, 50/60eye). Cond: GOOD. Quantity available: 20. Rare find. \$65 each or best offers. FOB; GOLD paper return address labels w/w/o call (500) \$2.00 ppd or details SASE: D. Testa Jr., 390 Lincoln Ave. RJ, Newark, NJ 07104.

HAL DS-3000/V2 \$850, ST-6000S \$399. Kenwood TL-922 2KWPEP linear, 80-10 meters (new) \$999. WA50XK, 2519 Holiday Dr., New Orleans, LA 70114. Days; (504)367-8649, Nites: 392-9101.

ELECTROSENSITIVE FAX paper \$4 roll (19" x 450') TS- 1060 (\$25), HO-10 (\$50), HP-400 (\$25), HP-415 (\$20), HP-430 (\$20), RCA voltohmism (\$30). ALL FOB. W6UBS, (714)462-6316.

R390A's BY Collins and other manufacturers. Checked and aligned \$250.00 and up (714)222-9446, WB6VBL, 1135 Alexandria Dr., San Diego, CA 92107.

TELETYPE MANUALS - Model 28ASR, 3-volume set \$24.50 plus \$1.00 postage. Manuals also available for Model 15, 19, 32, 33, 35, plus thousands of others on military surplus receivers, transmitters, test sets. Send 50c (coin) for large list. S. Consalvo, W3IHD, 7218 Roanne Drive, Washington DC 20021.

COMPONENT UPDATE. All UT-4 components and programmed Proms per January and February ads. Reprint of UT-4 Trouble-shooting articles (1976/77 Journal) \$1.00 postpaid, courtesy airmail overseas. Peter Bertelli, W6KS, 5262 Yost Place, San Diego, CA 92109. 714-274-7060.

FACTORY ASSEMBLED ST-6/AK-1 AFSK with UT-4 terminal unit/speed converter/buffer. A real work horse and in excellent condition. \$450 or best offer ppd. Write Dean Mellstrom, WB6JNV, 1612 Big Dipper Way, San Diego, CA 92073.

TU POWER Transformer. 115 volts primary, 250 volts center tap at 60 ma and, 28 volts center tap at 500 ma secondaries. \$10, includes shipping. Midnight Engineering Group, P.O. Box 349, Galesburg, IL 61401.

MODEL 28 ASR Teletypewriters \$350-\$375. RO Consoles \$175. Paper winders \$35. RO - 3-speed teletypewriters \$175. Tape perforators \$50, much more. State your wants. Sens SASE for partial list to: GOODMAN, 5454 South Shore Chicago, IL 60615, (315) 753-8342.



P
R
I
N
T

N
O

E
V
I
L

TH-5 TELETYPE TERMINAL UNIT REVISITED

This compact military unit, containing 15 tubes, supplied 20 ma of magnet current for a receiving and transmitting system operating on 1325 (Mark) and 1225 (Space) signals. It can be readily modified to receive and transmit with AFSK at 170 Hz shift in amateur service. Components are plainly marked, generally on two swingout boards mounted with screws. Instruments required to modify are a counter, an audio signal generator (use your receiver xtal calibrator, setting the tuning control for the desired audio frequency), a VTVM or multimeter and an open circuit phone plug. Capacitors used for tuning should be mica or mylar of 300 volt rating. All work is referenced with the unit upside down, front panel near you.

POWER SWITCH.

Remove the RING switch, clip all wires, insulate each end (daub with fingernail polish). Mount a SPST toggle switch in this hole and run one wire of the power cord through this switch.

TO CHANGE THE AFSK FREQUENCIES. (Right hand board).

1. Remove the R 50 resistor and replace it with a 1 megohm resistor A3-B3.
2. Remove C 36- bottom side A8-B8.
3. Remove C 34 A5-B5.
4. Adjust both screwdriver slots of C 30 to point toward the panel.
5. Connect counter to Posts 4W-S. Place function switches in 4W and SEND. Apply Power.
6. Add capacitors to replace C 34 to produce as nearly as possible 2295 Hz. About 1800 mmfd is required. Stop a few Hz above 2295. Adjust both sections of C 30 for 2295 Hz. Remove power.
7. Using the topside terminals A8-B8 replace C 36 with about 1900 mmfd. Insert the open circuit phone plug in a SEND jack. Apply power. Adjust C 36 for 2125 Hz as near as possible. C 30 varies both the 2295 and 2125 Hz signals so that you may be able to split a small (3-5) Hz difference. Turn off power.

TO INVERT THE AFSK FREQUENCIES FOR AMATEUR CONVENTIONAL SHIFT

8. On bottomside of right hand board, term B 10, cut and tape BLUE-WHITE wire (R 53).
9. Same board, term D 10, remove WHITE-ORANGE-BLUE wire and solder to term B 10 (R 53).

TO REDUCE THE OUTPUT LEVEL.

10. Jumper Posts E-4 (SEND) and E-6 (RCV) and ground.

11. Lift lead on E-3 (SEND); connect to one lead of 1/2 watt 510 ohm resistor. Connect 10 ohm 1/2 watt resistor to other lead of 510 ohm resistor and ground (E-4). Connection junction of two resistors to E-3. This results in about 15 millivolt output, if too high for your transceiver (using setting of mike control as reference), reduce the value of the 10 ohm resistor.

TO ELIMINATE CARRIER SUPPRESSION AND DECREASE DISTORTION IN AUDIO SIGNAL.

12. Remove tube V-11.
13. Clip R 46 from F-3 (bottom right hand board).
14. Remove R-69 (D16-F16 r.h. board). Replace with 1500 ohm 1/2 watt resistor.
15. Clip R-70 (D16-F16).
16. Remove jumper F4-D4 if installed.
17. Remove leads from Pin 6 of V 8, solder and tape.
18. Clip R 71, D14-F14, C-44 at A-26.
19. Tube V 15 serves no purpose and may be removed.

DEMODULATOR MODIFICATION (left hand board-power off).

20. Remove V 7 Tube and V 6 tube. this defeats the original purpose of neon lamp E 9 which now becomes a pilot lamp. It also eliminates the receive low signal gate.
21. Jumper U-7 to U-12. Clip R 23 at U-10, R 22 at U-7, R 30 at X14.
22. Install some type of binding post or test lead socket in one of the ventilation holes on the front panel above the RING switch side. Connect an 0.01 mfd capacitor to ground. Connect a 1 megohm resistor through a lead to terminal Z-9 (top or bottom of board).
23. Locate the two stacks of transmitting type capacitors on the right hand top side of the chassis. Remove the left hand board.
24. Remove both stacks. There are nuts on the bottom side, re-install the screws with the heads on the bottom side and nuts on topside. Be sure to use the insulating washers, flat washers and lock nuts. Mark on the chassis top, the designations C-14-C-15 and C 10-C11-C12.
25. Install the capacitor removed from C 12 (0.02 mfd) on the inboard screws marked C14-C15. Add a soldering lug between a pair of nuts on each screw on topside of chassis. Replace l.h. board.
26. Remove tube V 5.
27. Connect the audio generator and counter to terminals 4W-R.
28. Connect a DC voltmeter Positive (start with a high range setting) to the new test jack and ground. If a VTVM, offset the ZERO control to make the hand be about center scale. If a multimeter, watch

polarity closely when the unit is turned on; reverse if necessary. Short or jumper the screws for C10-11-12 (outboard).

29. apply power. Set the audio frequency to about 2500 Hz. Increase the level until the meter responds to the signal.

30. Tuning the audio generator from a higher frequency, determine the resonant frequency peak by closely watching the meter. this is broad, but patience will allow determination within one minor scale division on the meter. The frequency should not be lower than 2295 Hz but as high as 2335 or so is acceptable. The 0.02 mfd capacitor may be added to if necessary. If the frequency peak is too low, then remove and build a stack to meet this requirement. Use as sensitive a meter range as possible. Watch your fingers, there are high voltages present and the AC voltages on the screws is high.

31. Turn the audio level to off.

32. Reverse the meter leads (multimeter). Remove the short from C 10 and place on C 14.

33. Connect an 0.02 mfd capacitor to terminals for C 10. Increase the audio level. Tuning from a higher audio frequency, determine the resonant frequency and adjust the value as necessary to obtain not higher than 2125 Hz nor lower than about 2075 Hz.

34. Remove the short from C 14. Vary the audio frequency carefully. The meter should read zero (crossover) at close to 2110 Hz. The maximum voltages-positive versus negative-should be similar but is not critical. Remove power, reduce audio level to zero.

35. If it is necessary to have more than 20 ma magnet current as for a Model 15-19, with magnets connected in series at 30 ma, locate the grey or black large size resistors in the center of the bottom of the chassis. Parallel resistors to make a total of 10,000 ohms of at least 10 watts and add to the left hand resistor.

36. Re instal tube V 5. Arrange to monitor the current at the receive jack.

37. Apply power (observe polarity of current meter-reverse if necessary). The current should be about 20 ma or 30-35 ma if modified. Insert the open circuit phone plug in one SEND jack. The current should drop to zero. If not, determine if the HOME COPY jumper is in place across D5-F5. If at some later experience with the TH-5 in use, the home copy does not work properly, parallel a 100,000 ohm resistor at R 41, B25-F25. Remove the phone plug.

38. Increase the audio signal input level. Vary from 2125 Hz to 2295 Hz. The current meter should change from some value to zero. At 2110 Hz, the meter may indicate a

CONTINUED

small current because the output tube is not operating as an ideal switch, however the magnets should have dropped out a current much above this value.

TO USE THE TH-5.

39. Connect the CONT leads to the PTT leads of your transceiver. Connect the 4W-R posts to the 500 ohm audio output. If only 8 ohms is available, insert a small 8 ohm voice coil to 500 ohm line transformer. Connect the 4W-S posts to your microphone input leads. Probably a new input plug is desirable. Observe ground leads and use shielded cable.

40. Plug your machine magnet plug into the RCV jack and the keyboard plug into the SEND jack.

41. This modification uses the transceiver in the Lower Sideband position for transmit and receive and is compatible with two meter FM.

42. For a receiving indicator, use the 'Flipping Line' type scope indication. Almost any scope should be useable. Set the horizontal sweep to show three or four intermingled 'X' shaped lines (120 Hz sweep or so) when you touch the vertical input with your finger. Connect the scope vertical input to the new test jack. Using a VTVM with the ZERO offset to center scale is also acceptable. With the receiver audio gain at zero and the terminal unit operating, set the vertical gain control for about one inch positive deflection. Insert the open circuit plug in the SEND jack. The trace should momentarily jump negative about the same amount. Repeatedly hitting a keyboard key should produce a pattern of horizontal lines connected by random interconnecting lines. If the scope has a DC input, some of the jumpiness of an AC only scope input is reduced, but is not a requirement. To tune in a receive signal, center the horizontal lines about equally above and below a reference line, a meter should hover near zero. Receiving should be possible in either NORM or REC positions of the function switch. When printing, tune the desired signal from a high audio tone until it starts to print. This is because the TH-5 does not have a band pass filter system in its input and harmonics of the received signals (if lower than the standard tones) can give erroneous outputs and only garble will print.

43. Activate your transceiver in the transmit mode (LSB). Put the function switch in the SEND position. Adjust the mike gain control for normal drive level. This RTTY signal is equivalent to an AM signal so be careful of the power input to the transmitter.

44. In the SEND position, it should be possible to obtain local or home copy. If while receiving a RTTY signal, the machine goes into FIGS or LTRS, when not desired, reduce the receiver gain

control to zero and operate the appropriate LTRS or FIGS key and the machine should return to the desired mode. If using separate receiver and transmitter and the receiver does not mute when the transmitter is on, it will be necessary to open the terminal unit receive input to obtain home copy.

PERFORMANCE

The characteristics of a TH-5 modified by W4YZ (AAM4YZ) are:

AFSK output frequencies — 2122 Hz and 2298 Hz, at 15 millivolts.

Input level to cutoff magnet current — 15 mv.

Input level to limit in amplifiers — 80 mv.

Straddle tuning 2210 Hz — narrowest shift giving print — 25 Hz.

Peaking signal input at 2125 Hz — narrowest shift giving print — 100 Hz.

Peaking signal input at 2125 Hz — print obtainable to at least 1000 Hz shift.

Modified TH-5 will normally stay in MARK except for extraneous signal effects.

Some of the preceding was obtained from a variety of sources.

J.H. MCADAMS W4YZ (Army MARS AAM4YZ)

"SECOND LOOK AT THE YAESU FR/?/RTTY CONVERSION"

Recently going through some older RTTY JOURNALS, I ran across an article by JA1BRK Tachio on conversion of the YAESU FR101 receiver mode switch to add the CW narrow shift (600 Hz) filter to the RTTY position (JAN 75).


As any FR101 owner has probably noticed, the RTTY mode selector is wired to USB. This makes it difficult and sometimes impossible to receive correct RTTY without the aid of a normal-reverse network in the terminal unit. Step 1 in the diagram changes the RTTY mode selector to LSB instead of USB. At this point, also note that the RTTY mode selector position has a wider bandwidth window than either of the normal sideband positions. Step 2, though working in limited space, is quite simple and involves the addition of two short jumper wires. Note that in the YAESU FR101 Manual, page 18, the cutting of the jumper wire between pins 6 and 7 of S3C wafer switch is not clearly defined. This step is the last step in switching the narrow cw filter up to that also of the RTTY mode position. CW and USB operation is not lost as a result of this conversion.

After completion, which takes maybe a half-hour for us slow pokes, I found that my disbelief of allowing the cw filter to pass a RTTY signal because of its narrowness was soon put to rest. Note: RTTY space signals do not pass through the normal wired CW-NARROW filter position.

This conversion is fantastic and I don't know how I got along without it? Because of the wider window bandspread in the RTTY position, the "new" RTTY filter not only passes all 170 Hz. signals, but actually acts like a whole different filter in sound when compared to the normal cw filter. In fact, I find that I am using the RTTY position now for extremely difficult QRM cw signals. One does not have to be a teletype-nut to take advantage of this conversion.

Mike Stone WBOQCD

schematic page 20

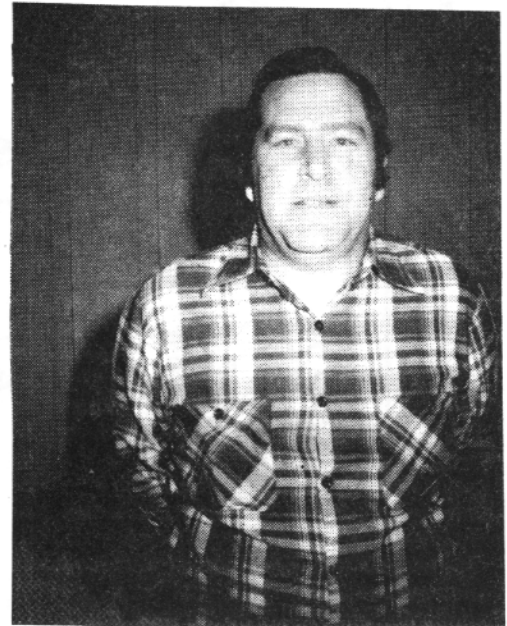


John P. Goheen III Editor

Murphy's Law
In any calculation,
any error which can
creep in will do so.


Any error in any calculation will be in the direction of most harm.

115V
(220V)


200-300 EACH SIDE C.T. 30-50 MA MIN.

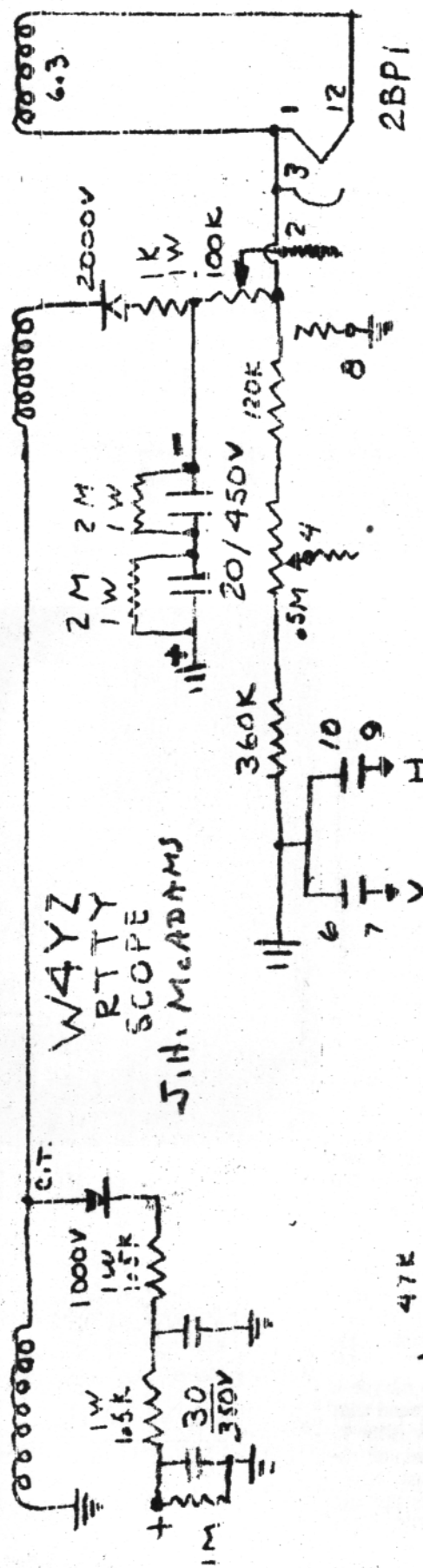


W4YZ
RTTY
SCOPE
J.H. McADAMS

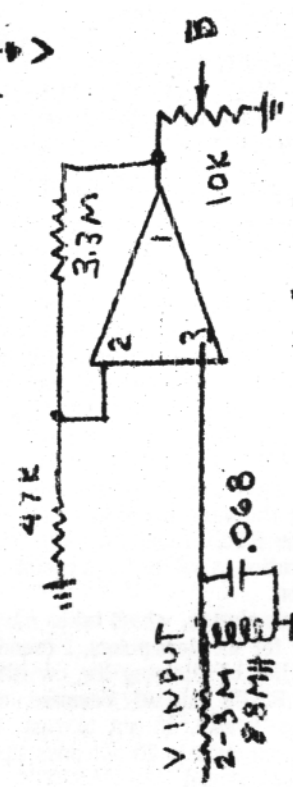

741 OP AMP
DUAL

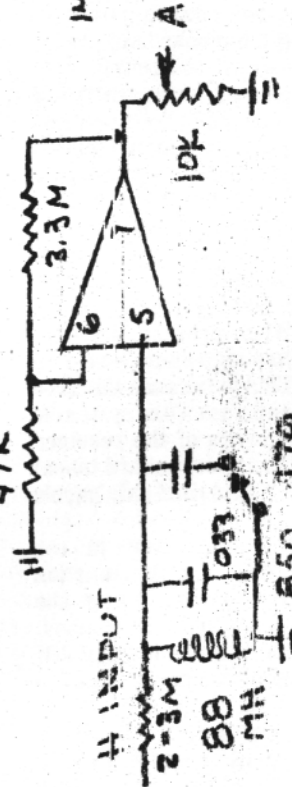

(INSIDE T.U.)





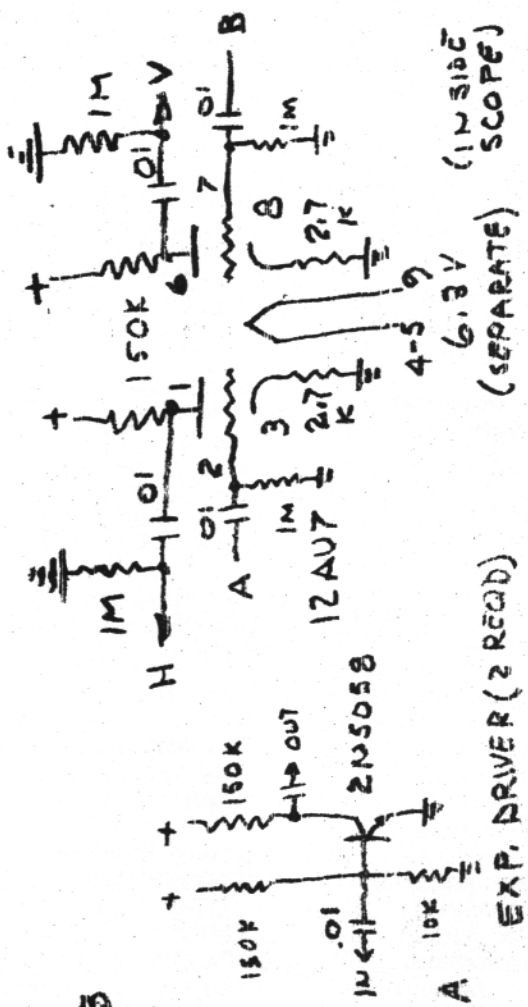


EXP. DRIVER (2 READ)
(SEPARATE)

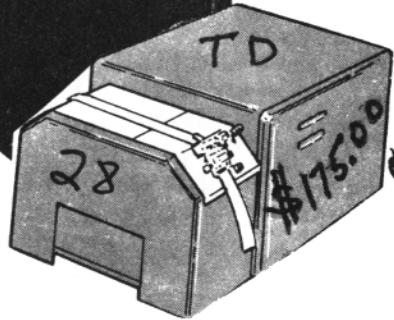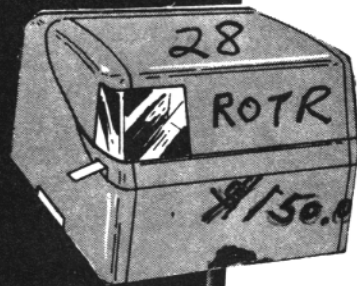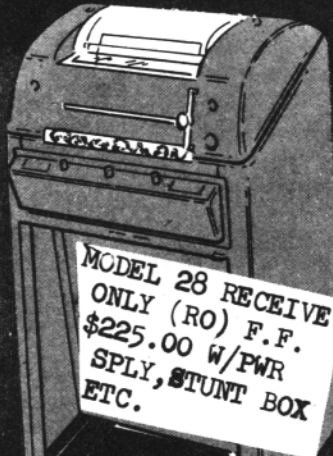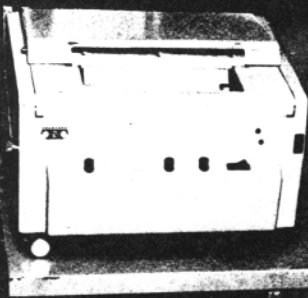
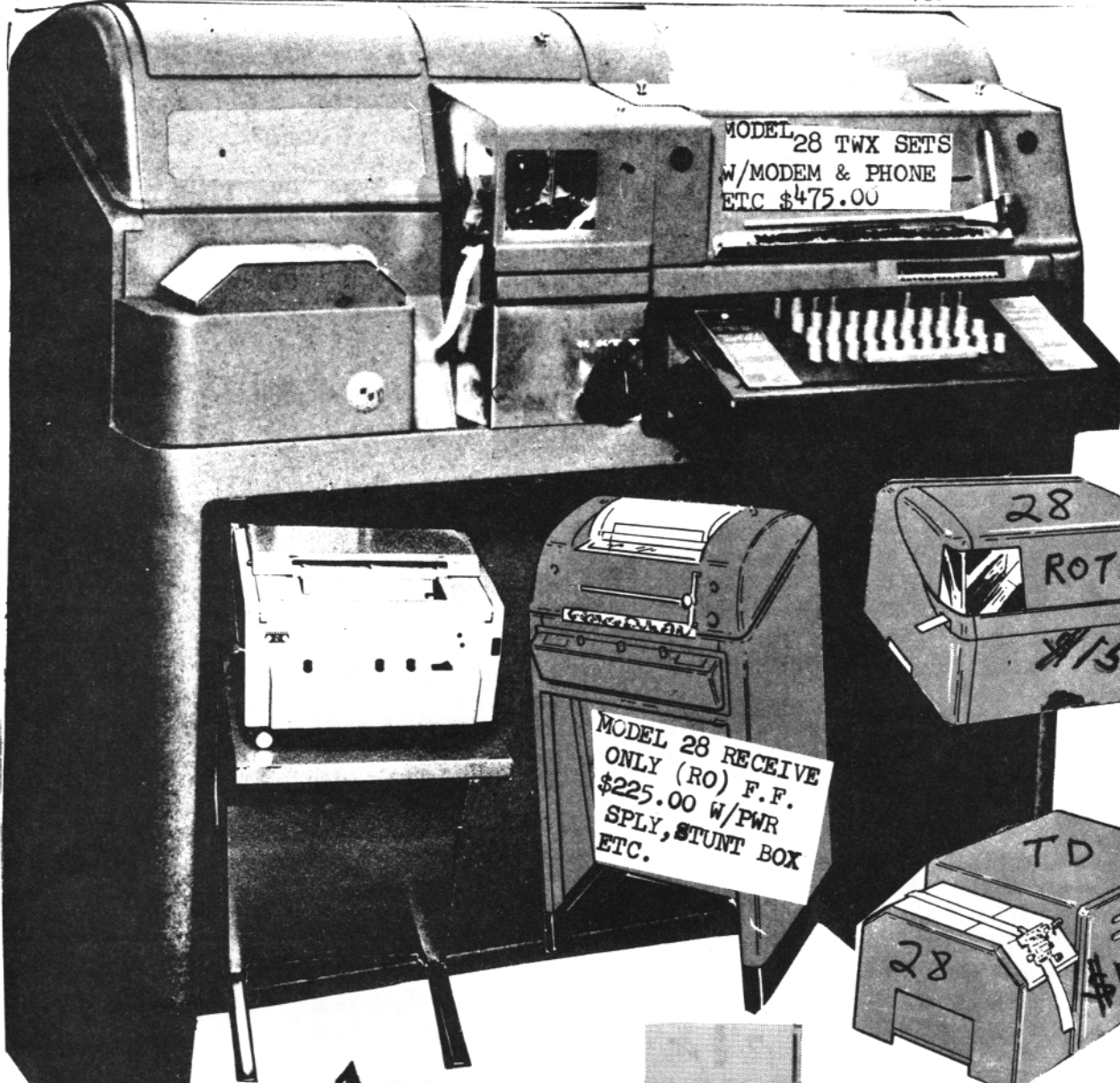
6.3V
(INSIDE SCOPE)

300V NPN
RADIO SHACK R52008 (274-2008)
ADJ. BASE VALUES FOR
EQUAL SWING AT OUTPUT
(REPLACE 12A U7)

MODEL 28 ASR (AUTOMATIC-SEND-RECEIVE) COMPLETE W/TD (TRANSMITTER DISTRIBUTOR), PWR SPLY, STUNT BOX, PERFORATOR ETC. SPECIFY SPROCKET OR FRICTION FEED \$375.00. IF A PRINTING PERFORATOR IS DESIRED ADD \$50.00. CRATING & LABOR ADD \$35.00.



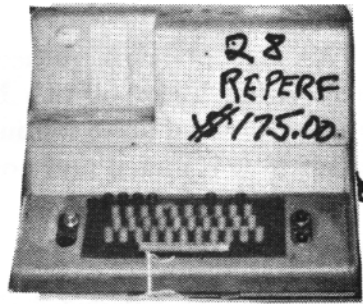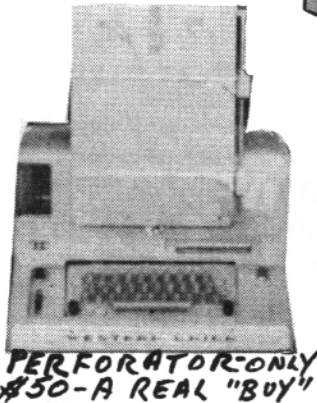MODEL 28 COMPACT W/SKIN TIGHT COVER. 3-SPEED GEAR SHIFT. RECEIVE ONLY (RO) F.F. 32/33 PEDESTAL CONTAINS A PWR SPLY, RELAY ETC. \$250.00. ALL ITEMS LISTED MFG'D BY TELETYPE CORP.



C.B. GOODMAN 5454 SOUTH SHORE DR. CHICAGO, IL. U.S.A. PHONE 312-753-8342 ANYTIME.

Qty & dealer disc't's. Prices are picked up Chicago. Add \$25 labor & crating or packing of RO, ROTR, REPERF., TWX \$50. Payment in advance-cashiers, certified or M.O. Have many items not listed, state your needs & wants-modems, data sets, paper winners, FRIDEN eqpt, manuals, schematics etc. Also 32's, 33's, 35's etc. Telex's etc. Antique telegraph and telephone eqpt. State your wants. CHARLIE

INTRODUCING. . .

COMPUTERIZED RTTY

INCREASE YOUR RTTY OPERATING PLEASURE WITH THE BTA-1 MICROPROCESSOR CONTROL CENTER FROM MS COMM - THE COMPUTER CONTROL PEOPLE SPECIALIZING IN AMATEUR RADIO PRODUCTS.

Our system directly interfaces to your existing Baudot or ASCII equipment - there is nothing else to buy. The BTA-1 exceeds the capability of the "FIFO-UART" system you're probably using now, while providing complete BAUDOT to ASCII and ASCII to BAUDOT conversion capability. The BTA-1 is easily installed. You don't have to be a microprocessor expert, as our device connects between your terminal unit and loop peripherals for complete RTTY control.

CHECK OUT THE BTA-1 STANDARD FEATURES

- UTILIZES STATE-OF-THE-ART 8085 MICROPROCESSOR DEVICES
- PROVIDES FULL BAUDOT-ASCII CONVERSION - USE AN ASCII KEYBOARD AND DISPLAY, OR CONVERT YOUR PRESENT FIVE LEVEL EQUIPMENT TO ASCII INSTANTLY WHEN THE F.C.C. ACTS
- CRYSTAL CONTROLLED SPEED GENERATOR ALLOWS "ON-LINE" 60 wpm TO 100 wpm CONVERSION
- UART QUALITY CHARACTER GENERATION IS PROVIDED BY THE BTA-1's TWO SERIAL-PARALLEL DEVICES. BOTH RECEIVE AND TRANSMIT SIGNALS ARE PROCESSED
- UNIQUE 1024 CHARACTER BUFFER (FIFO) ALLOWS MESSAGES TO BE PRELOADED-ALARM SOUNDS WHEN OVERFILL THRESHOLD IS REACHED
- AUTO ID - SENDS YOUR CW ID UPON DEMAND, OR EVERY TEN MINUTES WHILE YOU'RE ON THE AIR
- CANNED MESSAGE CAPABILITY ALLOWS INSTANT RECALL OF 165 CHARACTERS. MESSAGE IS ENTERED FROM YOUR KEYBOARD AND A FLIP OF A SWITCH PLACES THE ENTIRE MESSAGE ON THE FIFO FOR TRANSMISSION - ELIMINATES "RY" TEST TAPES AND EQUIPMENT OR PIX LISTS
- LED DISPLAY INDICATES AVAILABLE INTERNAL BUFFER SPACE
- 'SELCAL' AUTOSTART CONTROL - YOUR PRINTER REMAINS OFF UNTIL A PREDETERMINED FIVE CHARACTER SEQUENCE IS RECEIVED
- ALL FUNCTIONS ARE CONTROLLED BY TOGGLE SWITCH ACTION


The BTA-1 accepts FSK voltage level input available from most amateur terminal units and interfaces either 20 or 60 mA RTTY loops. All external connections are optically isolated for maximum safety and noise immunity. The BTA-1 RTTY control unit is available in kit form with quality 5"×8" PC board and complete instructions. A fully assembled and tested unit is also available. Power requirements are +5, +12 and -12 Volts.

CONTEST OP, PIX COLLECTOR, OR RTTY RAG-CHEWER, YOU OWE IT TO YOURSELF TO EXPERIENCE THE BTA-1 RTTY CONTROLLER.

Send us your QSL card for additional information about the BTA-1 and other microprocessor amateur products.

MS COMM - THE COMPUTER CONTROL PEOPLE Box 225 Greenfield, N.H. 03047

DOVETRON

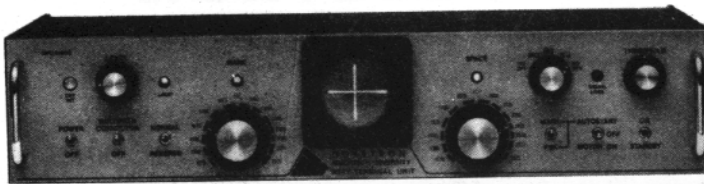


MPC-1000C

Multipath Correction
In-Band Diversity &
AFSK Tone Keyer

Amateur Net: \$545.00

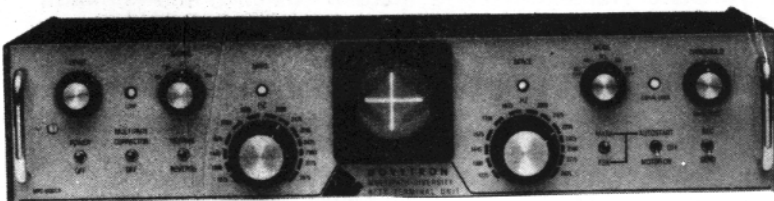Standard features include CONTINUOUSLY tuneable Mark and Space channels (1000 Hz to 3200 Hz), Dual Mode (MARK or FSK) Autostart and internal high level neutral loop keyer (20 to 60 ml). Both EIA and MIL FSK outputs are provided for direct interface to microprocessor and video terminal peripherals.



MPC-1000CR

Signal Regeneration &
Speed Conversion

Amateur Net: \$645.00

A front panel switch permits internal TSR-200 Signal Regenerator-Speed converter assembly to electronically "gear-shift" between 60, 67, 75 and 100 WPM. All incoming and outgoing signals are regenerated to less than 0.5% bias distortion. Also available with DIGITAL Autostart (TSR-200D): Amateur Net: \$695.00



MPC-1000R/- TSR-500

Dual UART Regeneration,
Speed Conversion, 20fJ
Char. Memory, Word Cor-
rection & DIGITAL
Autostart

Amateur Net: \$895.00*

The MPC-1000R/TSR-500 provides Preloading and Recirculation of the 200 character FIFO Memory, a keyboard-controlled Word Correction circuit, Variable Character Rate, Tee Dee Inhibit, Blank/LTRS Diddle, a Triple Tone-Pair AFSK Tone Keyer and a Character Recognition/Speed Determination DIGITAL (DAS-100) Autostart mode.

*The MPC-1000R is also available without a TSR assembly and functions as a MPC-1000C with a Triple Tone-Pair AFSK Tone Keyer. This "Basic-R" permits future expansion with a TSR-100, TSR-200, TSR-200D or TSR-500 by simply lifting the lid and plugging in the appropriate TSR assembly: Amateur Net (Basic-R): \$595.00

Your QSL will bring complete specifications, or call: 213-682-3705.



627 FREMONT AVENUE
(P. O. BOX 267)
SOUTH PASADENA, CA. 91030

MPC-1000R BY DOVETRON

MULTIPATH CORRECTION, IN-BAND DIVERSITY, SIGNAL REGENERATION,
UP-DOWN SPEED CONVERSION, 200 CHARACTER FIFO MEMORY,
KEYBOARD-CONTROLLED WORD CORRECTION & DIGITAL AUTOSTART



THE MPC-1000R REGENERATIVE RTTY TERMINAL UNIT

The DOVETRON MPC-1000R is a complete Transmit-Receive modem designed for optimum radio teleprinter communications on land, sea and in the air.

Standard features include a high level loop supply and keyer (neutral or polar), EIA and MIL FSK outputs, a phase-continuous AFSK Tone Keyer with three selectable Mark - Space - Shift tone pairs, Mark, FSK & Digital Autostart, Automatic Markhold, an internal RY Generator for terminal unit Self-Test and circuit adjustment, and a Signal Loss Alarm circuit.

The MPC Series is available in six different models to meet your exact requirements.

Complete specifications are
available on your request,
or call 213-682-3705.



627 Fremont Avenue
South Pasadena,
California 91030, U.S.A.

RTTY Journal

PO BOX RY

Cardiff by the Sea, CA. 92007

SECOND CLASS PERMIT PAID
AT ENCINITAS, CA 92024