cond. When a plug is inserted into a sax jack, the equipment where the those look is eventowed from the circuit and placed in series with the inserted plug. The original circuit is closed strongle another set of contacts in the sax jack, An and pack can be used to insert module requipment as circuit which may close through an activate which may close the sax jack, An and a circuit which may close the sax jack, An and a circuit which may be considered to the sax jack and a circuit which may be compared to the sax jack and a circuit program of the sax jack place in the sax jack place in the sax jack jack place jacks, place jack place jacks place jack place jacks place jack place jacks place jack p

12-28. The jacks used in communications are identified according to the number of centacist identified according to the number of centacist that are made or bruken when the plug is inserted in the jack. The tip and shower of the plug are not considered when identifying the jacks; in diagrams, only the context points indistantly in diagrams, only the context points indistantly the arrows are used. Figure 58 shows a plug inserted in a make-one, break-one jack. The schematic diagram of the jack and plug is shown so that you can easily identify the various parts.

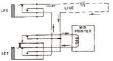


Figure 57. Teletypewriter jacks and circuits.

12-29. When special switching equipment (equipment which supplies power and testing facilities) is not necessary, a common switchbuard used at small installations is the SB-6/GG, shown in figure 59.

12.30. SB-6/GG. This switchboard makker possible direct connection of the signal line to teletypewiter equipment without patching or strapping. It also makes possible the interconnection of circuits coming to a particular station as well as allowing the softlines of special places of equipment to each line. The SB-6/GG or of equipment to each line. The SB-6/GG or operation of the state of the

12-31. This switchboard is designed for smally for connections that are to be made within a station operation and should be used primarily for connections that are to be made within a station. If it is necessary to expend the use of this switchboard, four of these switchboards are to connected together. Note, however, that four is the maximum number of SB-6/GGV that are to connected together for efficient operation, are not connected together for efficient operation.



Figure 58, Jack and plug showing internal connections.

12-32. The Sile-6/GG is constructed to hundle four outside signal lines and eight pieces of equipment. The switchboard has 16 jacks: 4 labeled "LEC-L," 4 labeled "JuS-2," 4 labeled "Set," and 4 labeled "JuS-2," All 16 of these jacks are make-before-break jacks; the LFO-1, LEC-2, and the sust; jacks are of the make-one, break-one type, and the set jacks are of the makes-two, break-box type.

12-33. The jacks are arranged in vertical groups so that there is an LPG-1, and LPG-2, and a 537 jack connected to every incoming signal line. In addition, there are four misse jacks that have no direct connection to the line.

that have no affect connection to the line.

12-34. SB-66/FGT. Another type of switchboard found in small continuorications installations is the SB-66/FGT (or K-6 push key cabinet).

This unit is a more complicated type of switching device than we have mentioned previously. By "more complicated" we mean that it is more diffi-

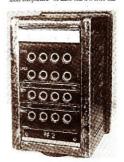


Figure 59. SB-6/GG switchboard.

cult for the mechanic to repuir and troubleshoot. However, because of its construction, it is much simpler to operate than a jackbox or an SB-6/66. The operation simply requires the depressing of the correct key to connect any one of the incoming lines to any desired piece of equipment.

12-35. The K-6 is a 36-key cablose, as skown in figure 90, desiyaed to handle a maximum of ski lines and six pieces of equipment. However, under many circumtenances you K-6's are ennected in multiple. This means that the signal lines are connected in series through two switchbard that will handle 12 pieces of equipment and 6 series through a switchbard that will handle 12 pieces of equipment and 6 serial lines.

12-36. The K-6 adds flexibility to station signal line and equipment connection. By this, we mean that in place of having only a certain piece of equipment on a particular signal line we can switch any prescribed number or type of machines to any of the incoming signal lines.

12-37. The X-6 can be mounted in either an unright position (on a wall) or in a last position unright position (on a wall) or in a last position (on a death or table), whichever is more convenied for operation. For maintenance on the switchboard or to prepare for line testing, the switchboard can be opened by removing two positions of the switchboard can be opened by the calculation of the switchboard can be also and equipment formum thought of the switchboard can be then and equipment formum though the switchboard can be then and equipment.

12-38. As stated previously, the K-6 can han-

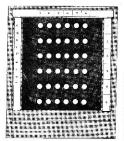


Figure 60. K-6 push key cabinet.

dle six signal lines and six pieces of equipment. Each one of these lines and pieces of equipment is represented by a row of keys on the cabinet. The horizontal rows (key bonks) represent pieces of equipment, and the verified (top-and-down) rows represent signal lines. To make necessary councerions, object-saing the key at the intersection of a line and an equipment row connect that piece of equipment to the specified inners that piece of equipment to the specified inners.


paces at cusponent to the specimen may be a first part of the packs. A large communications conter may use patch panels similar to the one shown in digree of. The patch panel is unsulfy located in the technical cannot section of the custor. A patch panel may consist of one or more custor. A patch panel may consist of one or more custor. A patch panel may consist of one or more custor. A patch panel may be part of the patch are approximately 20 im frames of section panels. The pack strings soom in figure of section panels of each page factor of the patch panels. However, the patch panels are provided with a fold-down tools. I floot wide, for use at a work ing seafned or as a base for portable test equipment.

12-40. All local conjument, incoming and equip lines and coloral and special creates are necessarily connected in the pioch panel via a main frame. This main frame is similar to those found in sciephose central offsets. As such, it provides a commental season for the grouping of creatist, local streams are provided with battery through the control of the provided with a comment of the provided with a summary of the provided with a comment ground return. This rockers the number of wires running to the puech panel and smithles toopheleshoring procedures.


12-41. Line and equipment receive (send) jacks. Referring to the jack field of our patch pagel in figure 61, we can see that the board is divided into several sections. The uppermost portion of the patch panel is reserved for special circuits. These jacks provide monitoring and patching capabilities for multiplexing, conference lines, dummy loops, and spare relay circuits. Twelve receive and twelve send circuit groups are available in this section of the panel. They are wired as shown in details A and B of figure 62. Note the types of Jacks used: the lower pair are LPG jacks, while the upper pair are called PATCH jacks. Also note that the circuit is a one-wire circuit with a common ground return. Insertion of a plug in the LINE REC jack, in detail A. places the tip of the patch cord in series with point I while the circuit to point 2 is opened. When a patch cord is inserted into the EQUIP REC jack, the cord is in series with point 2. while at the same time the circuit to point 1 is opened. The MON jacks may be used to place additional equipment in series with the circuit through the use of a patch cord. While both MON jacks seem to perform the same function, having two jacks in the same circuit makes it possible to monitor, both the LINE (point I) and the local

| LINE AND EQUIP REC JACKS | LINE REC | 0000 | LINE B | 000 | LINE SEMD EQUIP |
|-------------------------------------|-------------|--------|---------------|------|-----------------------|
| | EQUIP | | (EGUIP-%-< | | |
| | UNE | 0000 | 36063 0 0 0 0 | 1000 | HOR |
| | MON | 0000 | (000000000) | 1000 | |
| | EDUIP | | | - | EQUIP |
| 8 JACK RECEIVE CIRCUITS | LINE | 0000 | 1000000001 | 000 | LINE |
| | PATCH | 2000 | 000000000 | 000 | CRYPTO IN |
| | CRYPTO IN | | | _ | LINE |
| | UNE | 0000 | 1000000000 | 1000 | MON |
| | MON | 0000 | 10000 1 | 1 | CRYPTO IN |
| | CRYPTO IN | - | | - | CRYPTO OUT |
| | CRYPTO OUT | 0000 | (00000000) | 000 | PATCH |
| | PATCH | 0000 | 0 | ł | REC |
| | REC | | | - | CRACLO OTI |
| | CRYPT'S OUT | 0000 | 10 | 1 | HOW DO |
| | MON | 0000 | 110 | 1 | REC |
| | CONT | | - | } | CONT |
| REG CONT KEYS & | KEY | 0000 | 10 | 1 | KEY |
| | LAMP | 0000 | 110 | 1 | LAMP |
| SEND AND RECEIVE | REC | _ | | | REC |
| | LOOP | 0000 | 10 | 1 | LOOP |
| | SEND | 0000 | 10 | 1 | SEMO |
| | LINE IN | - |) | - | LINE IN |
| 8 JACK SEND C CIRCUITS | PATCH | 0000 | 10 | 1 | PATCH |
| | CRYPTO OUT | 0000 | 10 | 1 | CRYPTO OUT |
| | LINE IN | - 1 | - | | LINE IN |
| | MCN | 0000 | 1000000000 | 000 | WON |
| | CRYPTO OUT | 0000 | 0 | 1 | CRYETO OUT |
| | CRYPTO IN | | | } | CRYPTO IN |
| | PATCH | 0000 | 10 | | PATCH |
| | REPTD OUT | 0050 | 0 | 1 | REPTO OUT |
| | CRYPTO IN | | 1 | - | CRYPTO IN |
| | MON | 0000 | 110 | 1 | MON |
| | REPTO OUT | 0000 | 10 / | 1 | REPTO OUT |
| 4 JACK SEND CRCUITS | REC. | | | | REC |
| | PATCH | 0000 | 110 | 1 | PATCH |
| | SENO | 0000 | 10 | 1 | SEND |
| | REC | 1 | | 1 | REC |
| | MON | 0000 | 1)0 | (| MON |
| | SEND | 0000 | 10 | 1 | SEND |
| MISC JACKS CONT KEYS< & LAMPS | CONT KEY | 200000 | | 1 | CONT KEY |
| | LAMP | 0000 | 10 | 1 | LAMP |
| | Lique | 0000 | 10 | 1 | The same |
| | MISS | 0000 |)): |) | MISC |
| | 10000 | 0000 | 110 | 1 | 10000 |
| | MISC | 0000 | 10 | 1 | MISC |
| | | 0000 | 10 | 1 | 100000 |
| | MISC | 0000 | 0 | 1 | MISC |
| | 1 | 0000 | 1" (| 1 | 2000 |

Figure 61. Patch panel jack designation.

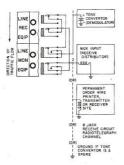

RECEIVE JACK CIRCUITS

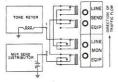

SEND JACK CIRCUITS Figure 62. Receive and send jack circuits.

equipment (point 2) at the same time-using separate units of equipment. The same is true about points 1 and 2 in the send tack circuits.

12-42. Eight-jack receive circuits. The next section of the patch panel is wired as shown in figure 63. The panel provides 26 groups of eight iacks for incoming lines. When you study figure 63 carefully, you see that we have four PATCH jacks and four MON jacks in each group of eight. By inserting a patch cord in the proper PATCH jack, we can place a specific portion of the circuit in series with the inserted cord, while disabling the rest of the circuit. Through the correct placement of patch cords in the MON jacks, we can monitor portions of the circuit without affect-

ine normal operation.

12-43. Control keys and lamps. Located beneath the eight-jack receive section is the receive key and lamp section of the patch panel. The patch panel is equipped with this section to provide for remote disabling of traffic teletypewriter equipment by technical controllers. Operation of the control key (CUT) on figure 63 grounds the receiving cryptographic equipment and causes it to remain in a steady marking condition. The associated lamp on the patch panel will glow when the key is operated.

- 12-44. While there are additional sections to the patch panel shown in figure 61, we will not discuss them at this time. Our main interests are the type of tacks employed and the method of wiring. Operation of the panel usually is the concern of the Technical Control section, while the original wiring to the main frame is normally performed by telephone cable splicing specialists, However, you may be called upon to troubleshoot and replace faulty jacks or wiring in the panel itself. Our coverage of the subject is sufficient to illustrate the use and wiring of the various types of jacks used in the patch panels found in
- teletypewriter communications centers. 12-45. Power and Signal Line Cabling. The responsibility of connecting a communications center to the required trunks and cables is not part of the job of the communications machine repairman, for it is a specialized job and requires a great deal of knowledge and skill. The job of running the lines required for small communications centers usually falls to Ground Electronics Engineering Installation Agency (GEEIA) personnel or, in some cases, it might be done by a local telephone installer. In either case, that individual must see that these lines are properly terminated within the communications center. This termination of lines will usually be to the switchboard mentioned. Running the lines of communications from the switchboard to the machines may then become the responsibility of the communications equipment repairman. If, however, there is a telephone installer available, it is usually best to have him run the lines within the center, since he has the knowledge and skill to do this iob much faster and easier.
- 12-46. If you cannot get a telephone installer to do the inside wiring of the communications center, it then becomes your job. The signal line connections between the switchboard and the machine are titled "inside wire runs" and should be connected in accordance with prescribed telephone installation procedures.

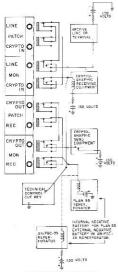


Figure 63. Eight-jack receive circoit.

12.47. Whe Runs. The inside wire run should follow a reasonably direct path from the switchboard to the machine location and should be free from obstuctions. It is better to select a longer route it, by so doing, you can avoid a concentition of pipes, electrical conjument, or moisture areas, which would be damaging to the wire. Select conditions where minimum maintenance is needed, and satisfactory service life is increased. These should be the deciding factors and are more important than the length of the wire run.

12-48. The appearance of the inside wire run is also important. In every situation a workmanlike job should be done and an effort made to see that the wiring job looks next. Thus, since a concealed wire run eliminates most appearance problems and some maintenance problems, you may frequently select a concealed wire route. However, in selecting and using such a route, you need a working knowledge of building spaces. For example, frame buildings generally have air spaces between the studs, and brick buildings may have an air space behind the inside wall. Where appearage or probability of wire damage is of sufficient importance, you may thread the signal line through these spaces. However, more rapid installations can be made by following a moulding or baseboard. Where installations are not suited for concealed runs or the time factor is to be considered, most wire runs must be made on the surface.

12-49. Several rules apply for surface runs. For example, it is better to follow the cailing line than it is to follow the baschoard of a room or basement. When running the wire in a room, use wire mouldings, picture mouldings, or raceways when they are available. It is best to place the wire in a metal or wood moulding on vertical runs, where picture or door mouldings are not accessible. Sometimes the moulding is needed to prevent damage. It is important to be sure that the inside wire does not interfere with the opcration of windows or doors. Also, the wire run should not snan open places or stair wells when these areas can be avoided. Beam-to-beam runs should not be made above workbenches or where boxes are stored unless the wire can be placed where it will not be clamaged. Where joists must be spanned, it is best to stay within 3 inches of the wall. Wire installation techniques depend upon the lob situation. Throughout the wire run, wire must have the proper clearance and protection. Where wire is secured to walls or goes through walls, floors, or ceilines, it is necessary to use proper fasteners and prescribed protection methods. The fasteners for inside wire are designed to fit almost all situations which you will encounter. However, remember to place the fasteners over studding in the walls and also never to fasten wires directly to conduits, pipes, or to pipe supports. The protection for inside wire is selected to suit the job at hand. You should maintain at least 6 inches between signal lines and foreign gound wires. However, this is not always possible, and some type of protection covering such as friction tape or porcelain tubing, should be used where the wires cannot be separated from other objects by the correct distances.